Topic of the project:

Project name: "ASIC design with open source tools"

Developing of an low resolution ADC. As example an 4-Bit ADC with conversion of the thermometer code into binary code.

Steps:

A small CMOS inverter with xschem and the sky130a technology (PDK) and simulate the circuit with ngspice:

Binary Logic level assumption

https://en.wikipedia.org/wiki/Logic level

Technology	L Voltage	H Voltage	note
CMOS	0 to 30% of Vdd	70% of Vdd to Vdd	Vdd = Supply voltage
	≈0.5 Volt	≈1.25 Volts	Vdd = 1.8 Volts

Preamp:



The above figure is the schematic for 15th threshold point of the analogue part of the ADC. The plot is as follows:


The inverter will switch from logic-low to logic-high when input voltage exceeds 1.785 volts. So, for this inverter the threshold is 1.785 volts.


For a 4-bit ADC we need 16 voltage level including zero (0 \sim 1.785 volts). The quantization should be 1.785/15=0.119 volts.


Vdd = 1.8 V


Th. 15: 1.785

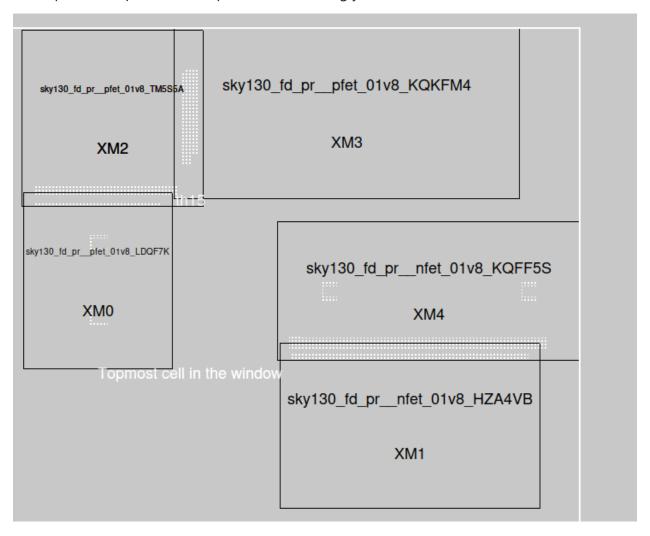For calculation the schematic and the plot already mentioned earlier. Remove all source to make symbol from schematic. As the symbol will have to be connected to Vdd and GND, those pins are replaced with Vp and Vn accordingly.



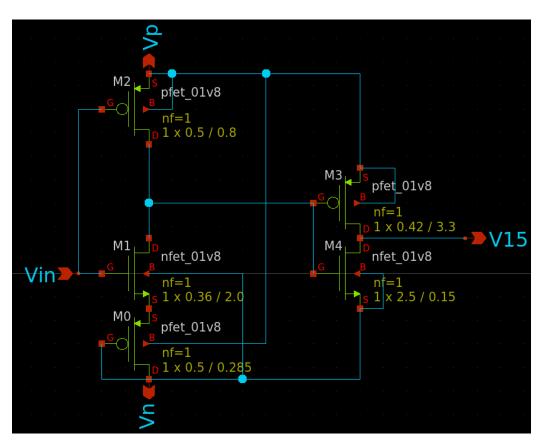


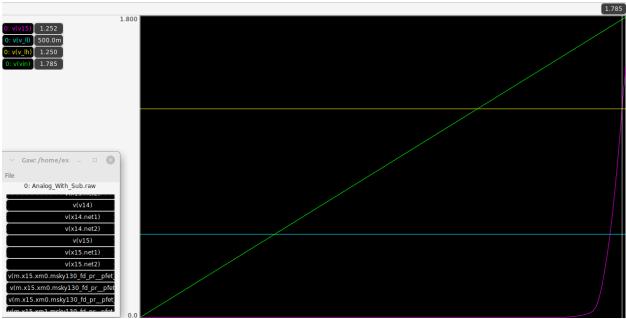

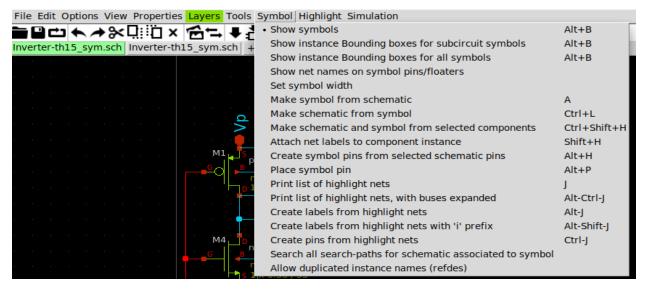




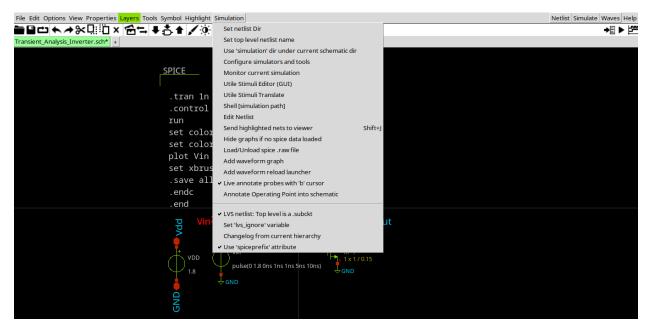
Magic=>before importing netlist to ngspice check LVS net




The simplified schematic is as follows:

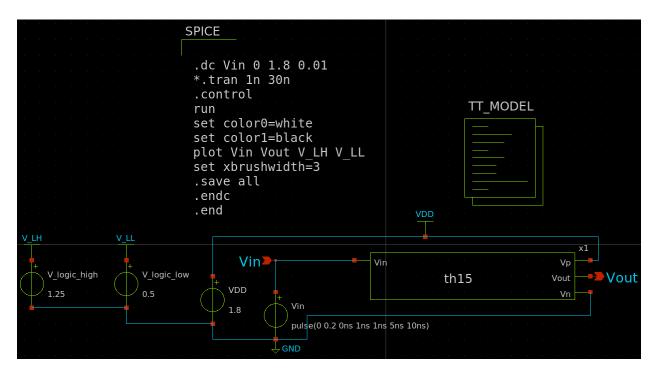


The plot is similar to the previous figure.

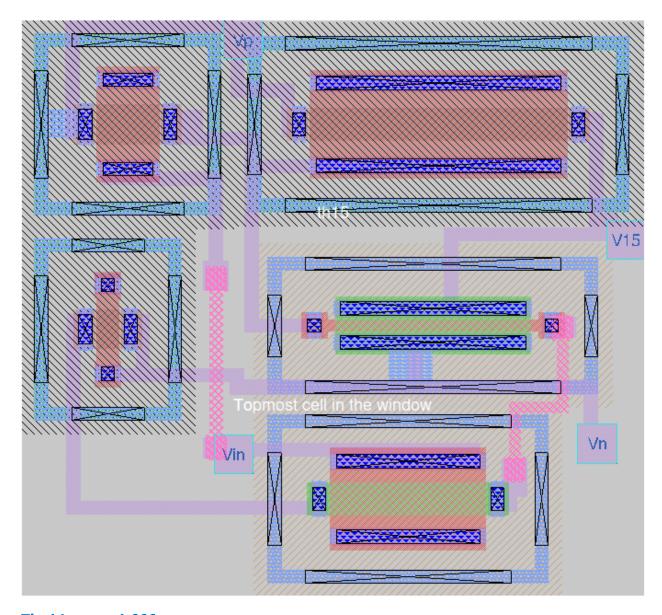


Th. 14: 1.666

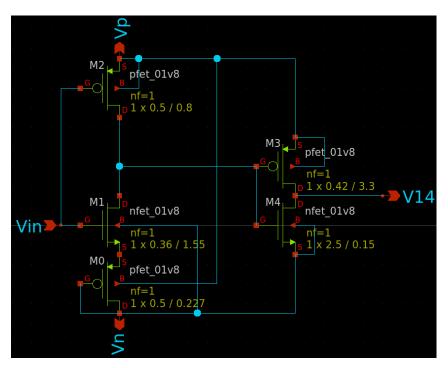


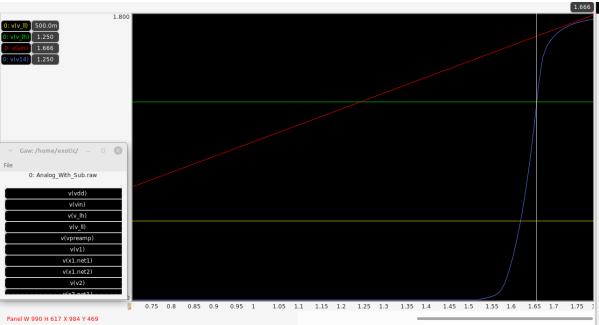



Rest of the figures are similar to the previous figures.

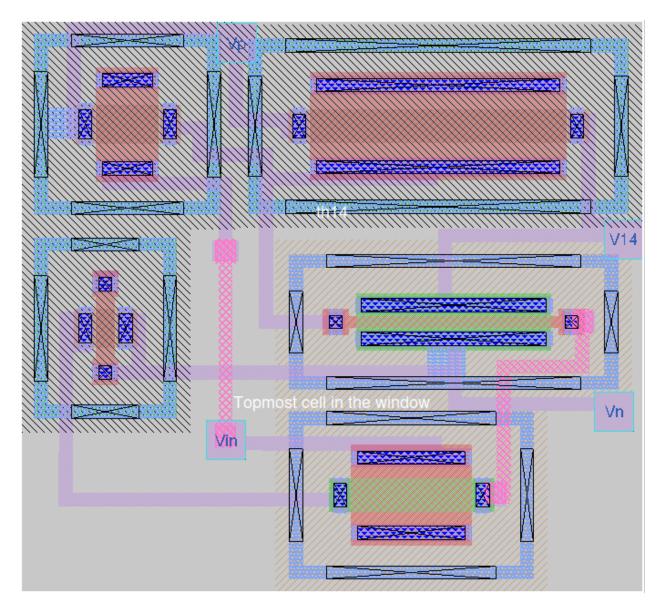


Th. 13: 1.547:

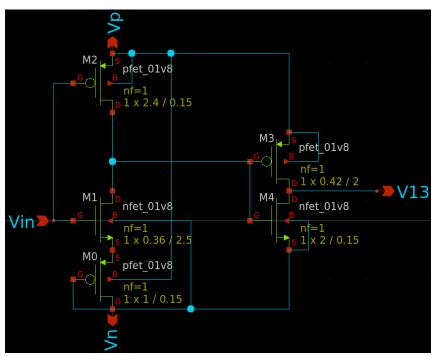


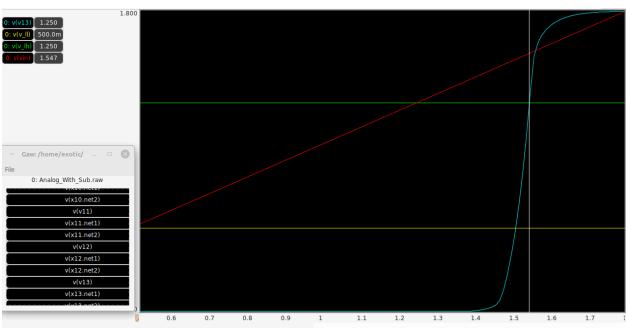

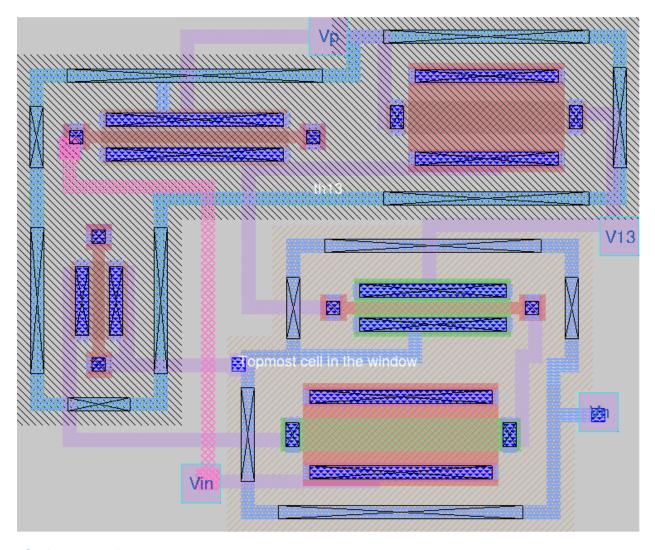



Th. 12: 1.428

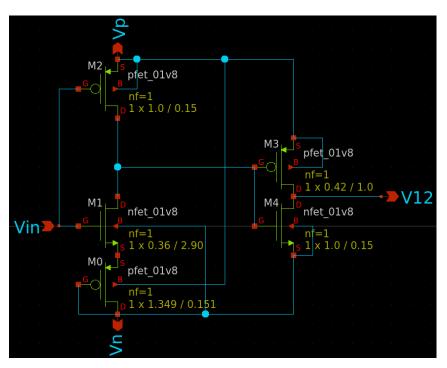

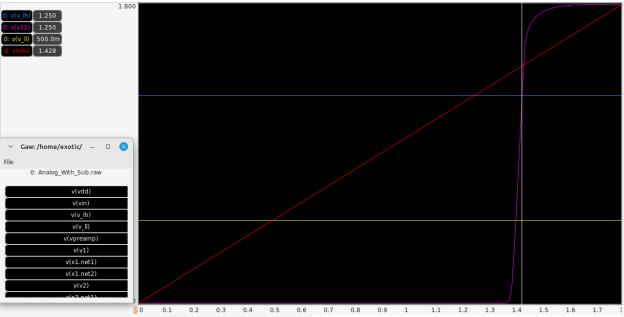



Th. 11: 1.309

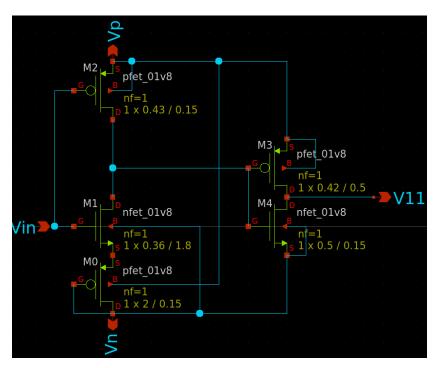


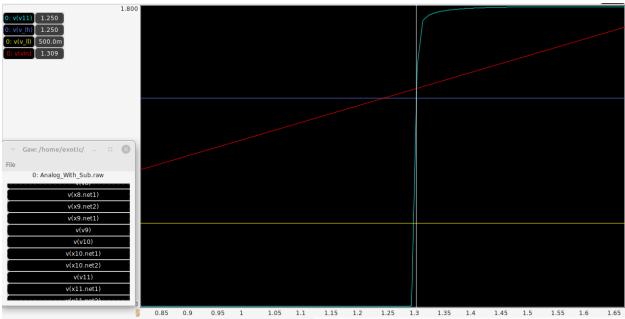


Th. 10: 1.19

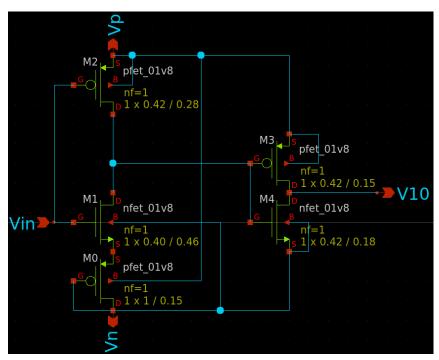


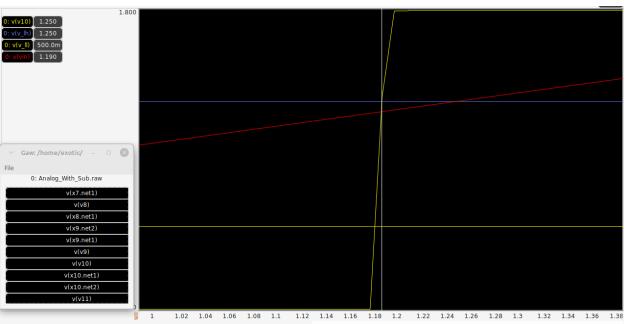


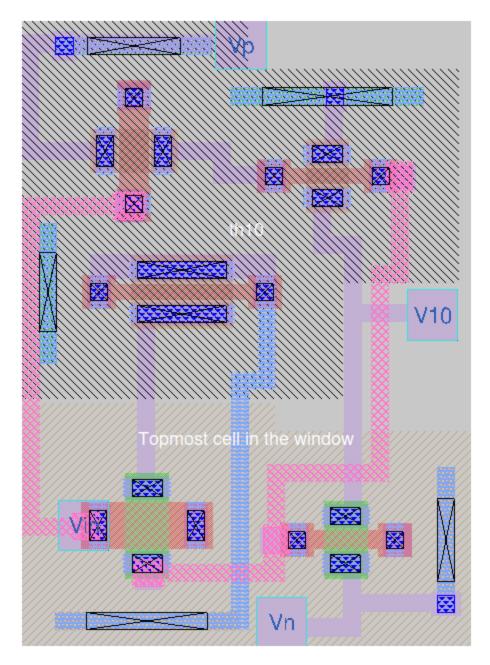


Th. 9: 1.071

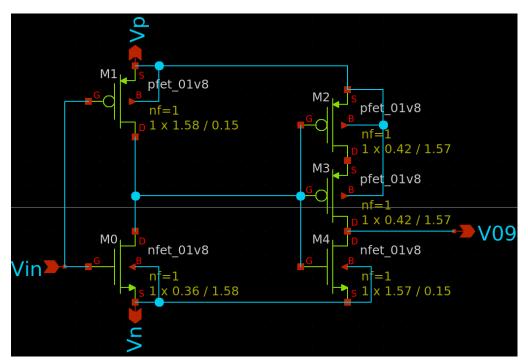


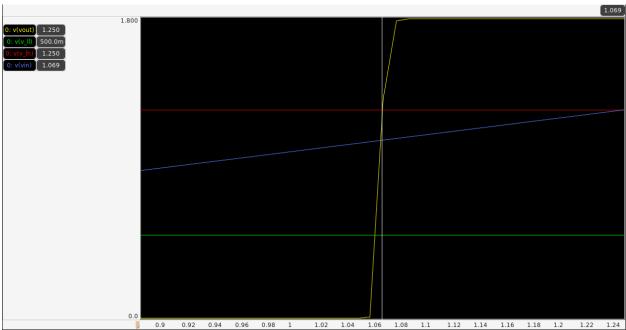


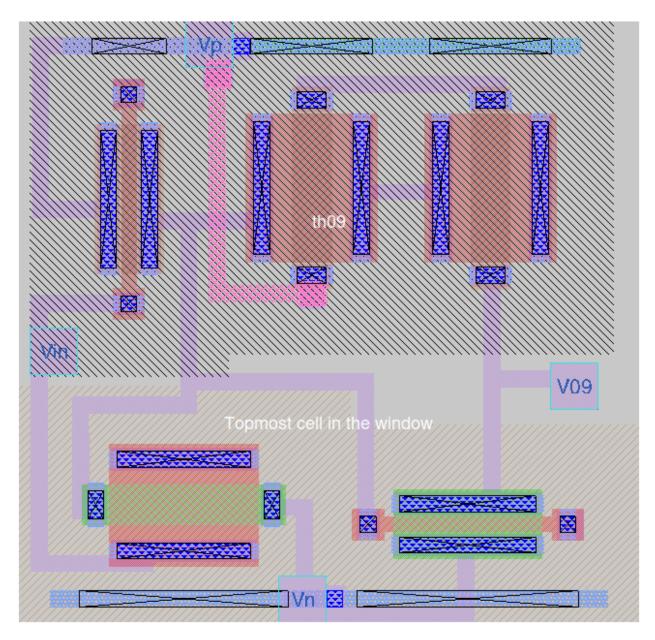


Th. 8: 0.9504

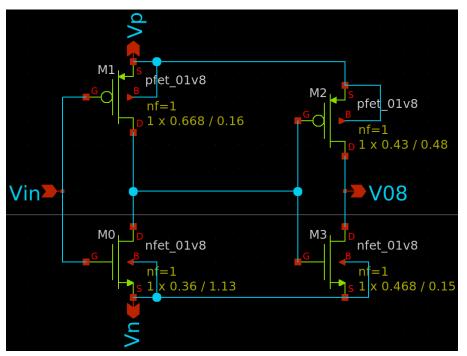


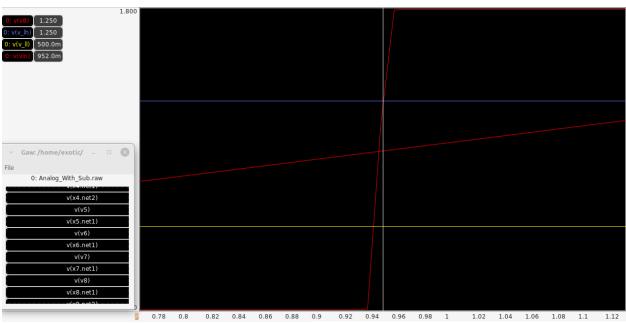


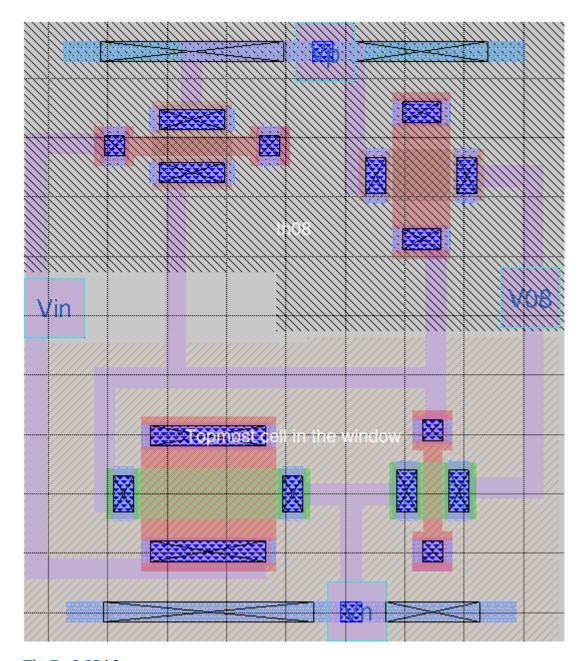


Th. 7: 0.8316

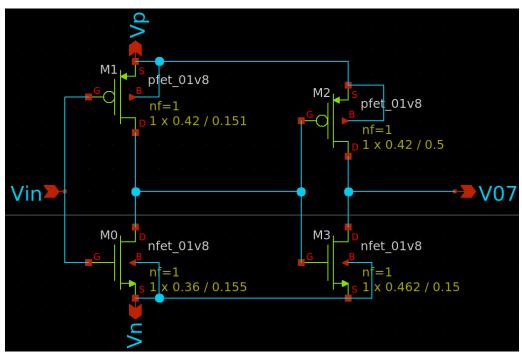


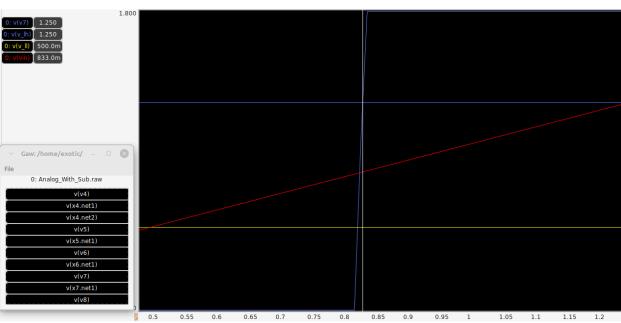

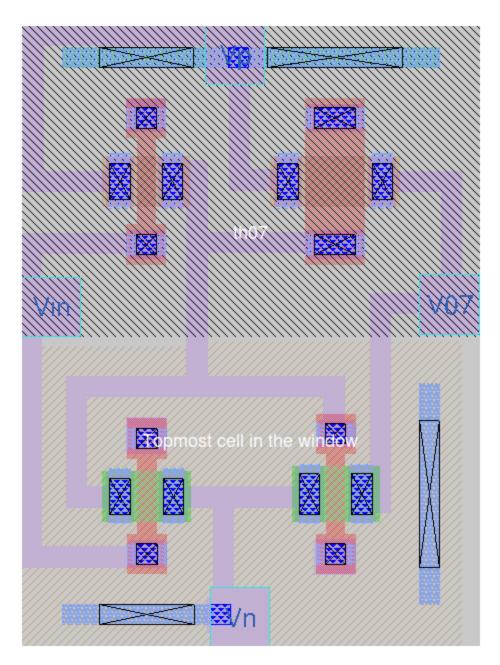



Th. 6: 0.7140

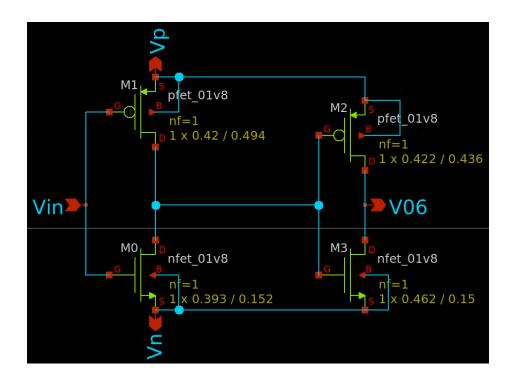


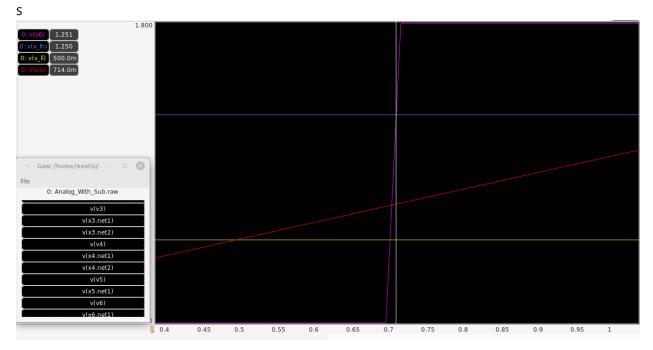


Th. 5: 0.595

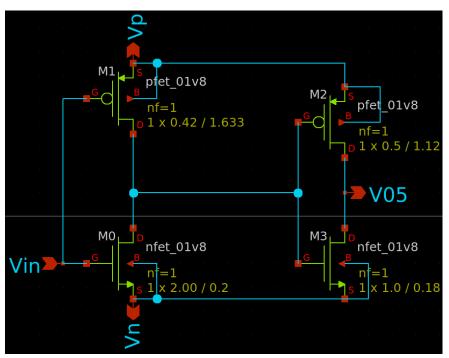


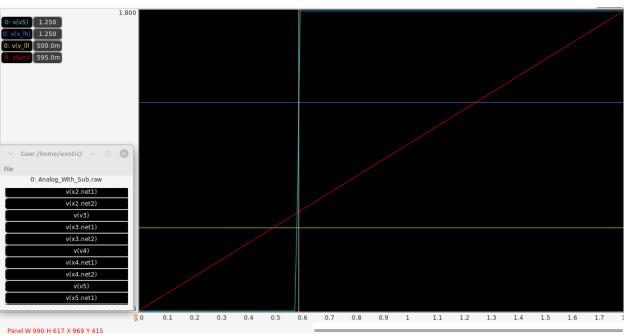


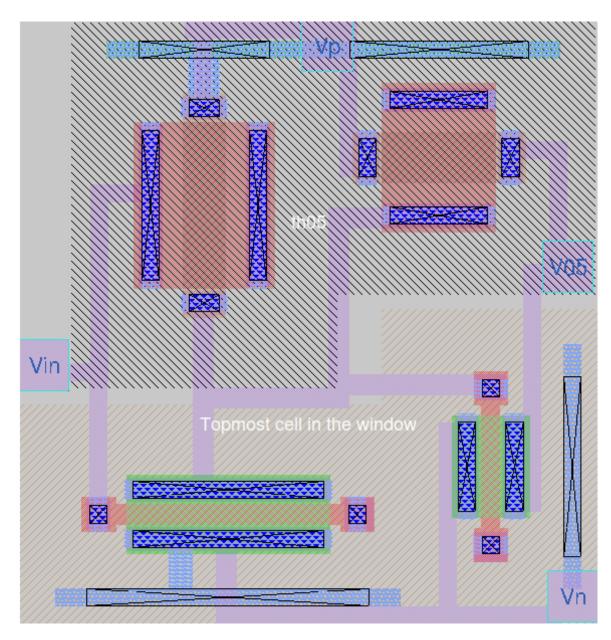


Th. 4: 0.4760

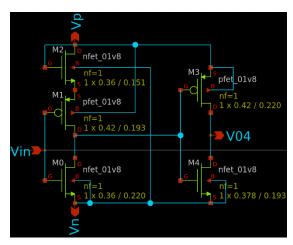


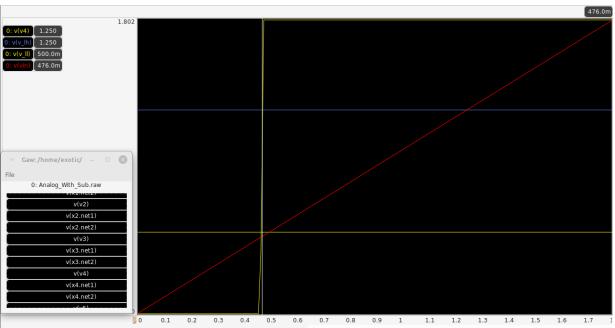


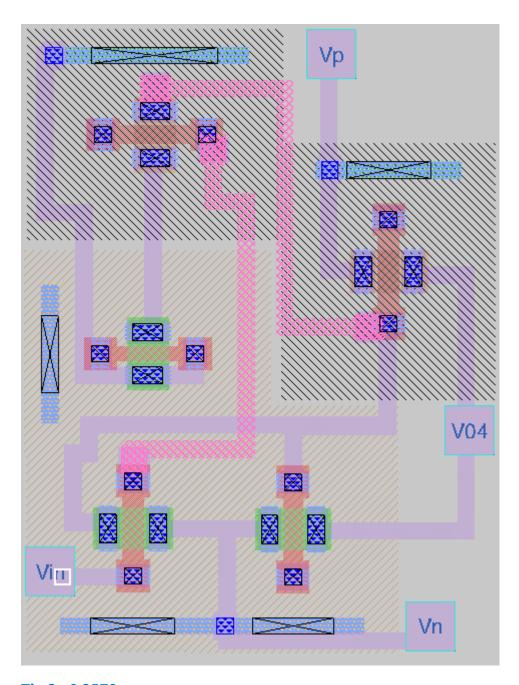


Th. 3: 0.3570

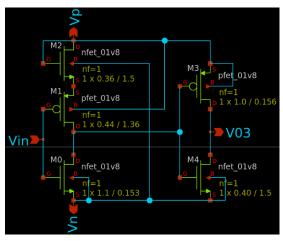


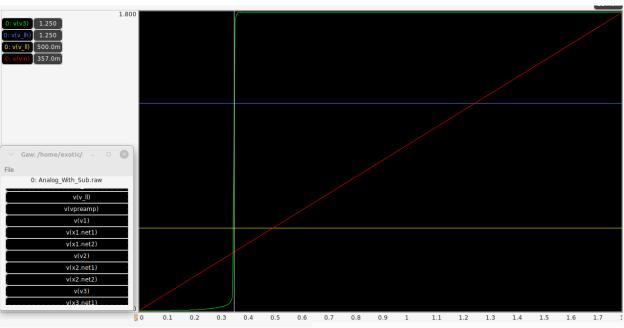


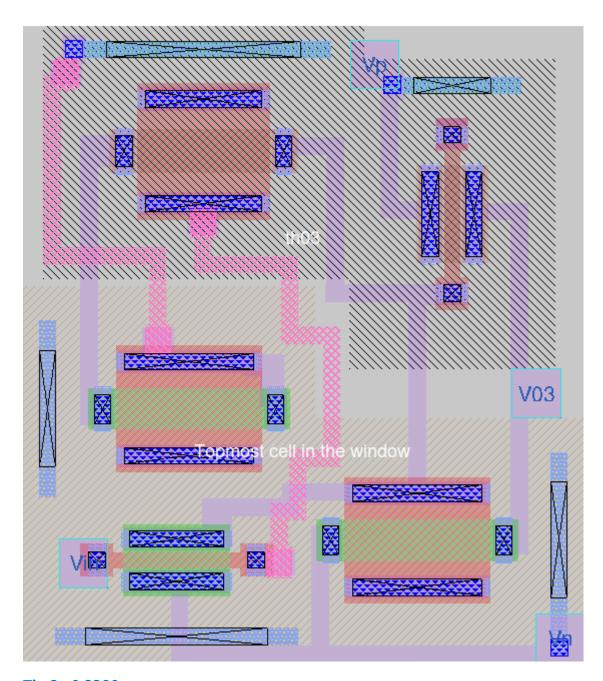


Th. 2: 0.2380

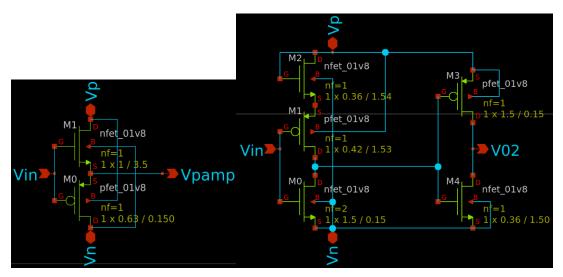

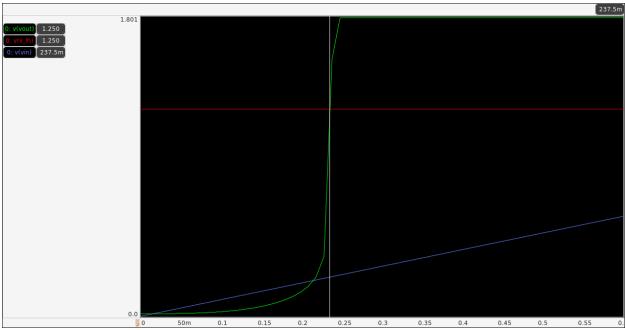


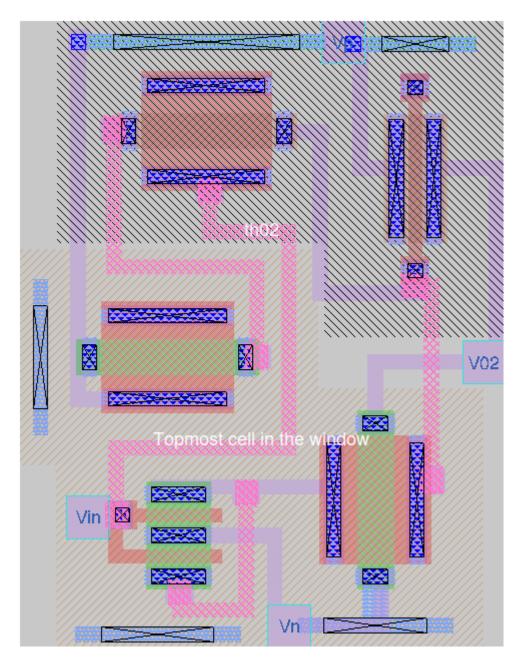


Th. 1: 0.119s

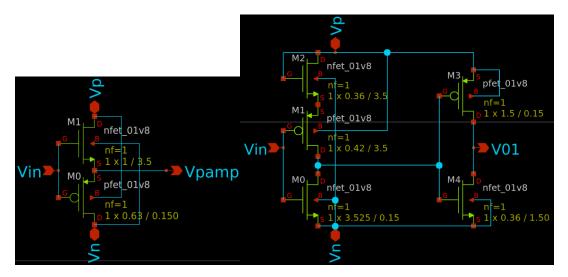


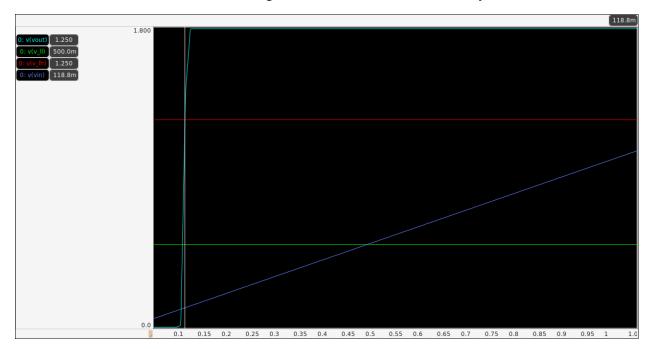
With combination of all thresholds the length and witdh need to be further adjusted.



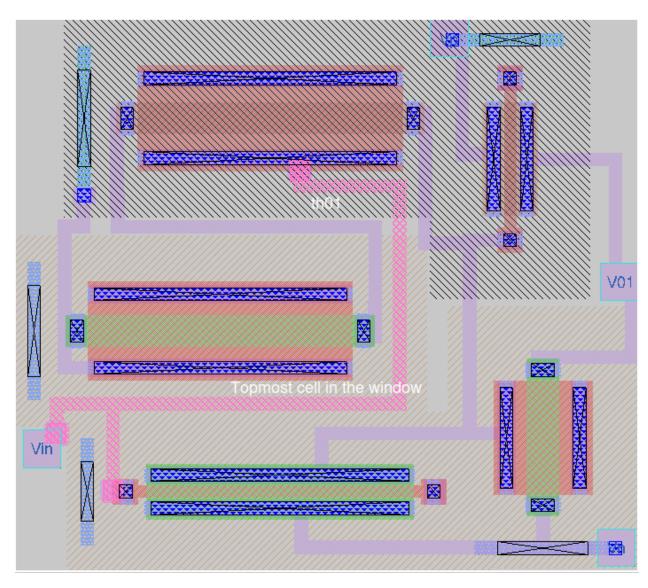

Combined Analog sch.

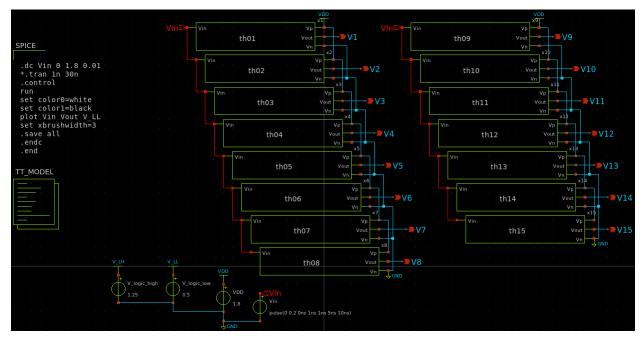

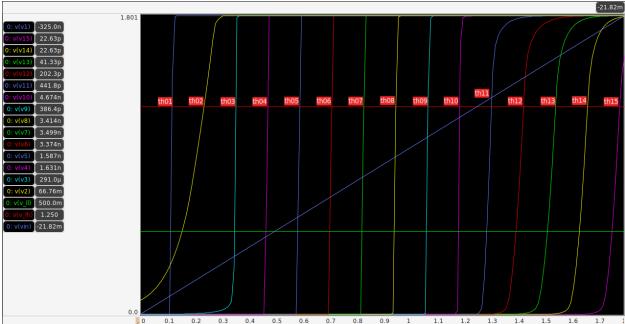

http://web02.gonzaga.edu/faculty/talarico/vlsi/xschemTut.html

https://ngspice.sourceforge.io/ngspice-control-language-tutorial.html

Alter subckt tutorial—

https://sourceforge.net/p/ngspice/discussion/133842/thread/5ad086c79f

https://sourceforge.net/p/ngspice/discussion/133842/thread/9a75acf2/#bf90/45b3/ea48

Pyspice ngspice interpreter

https://pyspice.fabrice-salvaire.fr/releases/v1.3/examples/ngspice-shared/ngspice-interpreter.html

https://github.com/ashwith/ngspicepy

Read spice raw output data

https://gist.githubusercontent.com/snmishra/27dcc624b639c2626137/raw/742fe0dd59c7b2c41b71a1c8c1c2506d13affc53/rawread.py

ngspice wrapper for python

https://github.com/eps82/lyngspice/wiki

write some verilog code to convert the thermometer code (from the inverter stages) into the binary code

```
module thermometer_to_binary (
  input [14:0] ith,
  output reg [3:0] binary
);
always @(*) begin
  case (ith)
    16'b0000000000000000: binary = 4'b0000; //~0.0000
    16'b00000000000000001: binary = 4'b0001; //\sim 0.1188
    16'b000000000000011: binary = 4'b0010; // \sim 0.2376
    16'b000000000000111: binary = 4'b0011; // \sim 0.3564
    16'b00000000001111: binary = 4'b0100; // \sim 0.4752
    16'b00000000011111: binary = 4'b0101; // \sim 0.5940
    16'b000000001111111: binary = 4'b0110; // \sim 0.7128
    16'b0000000011111111: binary = 4'b0111; // ~0.8316
    16'b000000011111111: binary = 4'b1000; //~0.9504
    16'b000000111111111: binary = 4'b1001; //~1.0692
    16'b000001111111111: binary = 4'b1010; //~1.1880
```

```
16'b000011111111111: binary = 4'b1011; // ~1.3068
16'b00011111111111: binary = 4'b1100; // ~1.4256
16'b00111111111111: binary = 4'b1101; // ~1.5444
16'b01111111111111: binary = 4'b1110; // ~1.6632
16'b1111111111111: binary = 4'b1111; // ~1.7820
default: binary = 4'bxxxx; // Don't care
endcase
end
```

endmodule

http://www.asic-world.com/verilog/veritut.html

https://nandland.com/introduction-to-verilog-for-beginners-with-code-examples/

https://www.youtube.com/playlist?list=PLfGJEQLQIDBN0VsXQ68_FEYyqcym8CTDN

https://github.com/Swagatika-Meher/msvsd2bitcomp

ALIGN Tool-

https://www.youtube.com/playlist?list=PLvXKBnlvcSm30Y0zu1765oG x-ECU8tVG

https://github.com/syedimaduddin/msvsd4bituc/tree/main/Week-1

https://github.com/ALIGN-analoglayout/ALIGN-public

https://learning.edx.org/course/course-v1:HarveyMuddX+ENGR85A+3T2021/home

https://www.vlsiuniverse.com/digital-thermometer-code-in-verilog-vhdl-flash-adc-binary-encoder/

https://www.classcentral.com/subject/vlsi?free=true

https://www.eng.biu.ac.il/temanad/digital-vlsi-design/

https://www.youtube.com/playlist?list=PLZU5hLL_713x0_AV_rVbay0pWmED7992G

https://youtu.be/BlqLk23hE90?list=PLZU5hLL 713x0 AV rVbay0pWmED7992G

get familiar with the yosis syntesis tool to convert the verilog code into a CMOS circuit

https://www.mehmetburakaykenar.com/synthesis-n-bit-counter-with-open-source-yosys-synthesizer/294/

https://github.com/spdy1895/RTL synthesis using sky130

https://github.com/Imellal/RTL-workshop-Sky130-PDK


After install YoSys (see the bash file in the repository), run the following commands—

>> yosys // open yosys console in terminal


>> read_liberty -lib

/usr/local/share/pdk/sky130A/libs.ref/sky130_fd_sc_hd/lib/sky130_fd_sc_hd_tt_025C_1v80.lib

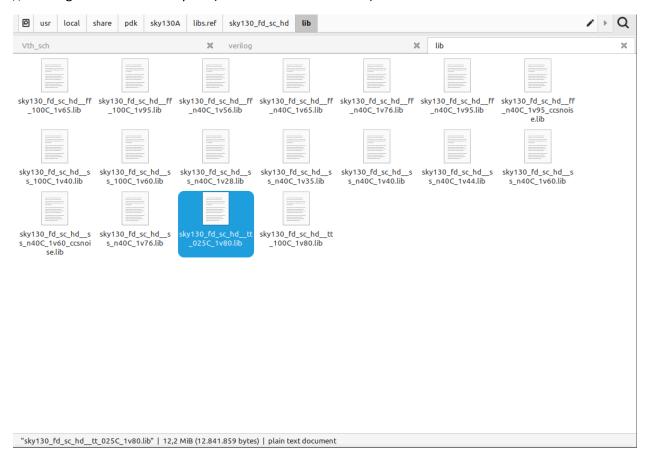// reading the suitable liberty file (see the screenshot below)



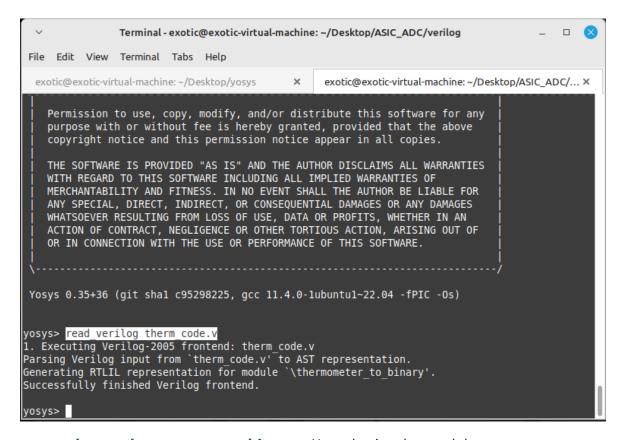
>> read_verilog therm_code.v // read the verilog file



>> synth -top thermometer_to_binary // synthesize the module

```
>> abc -liberty
/usr/local/share/pdk/sky130A/libs.ref/sky130 fd sc hd/lib/sky130 fd sc hd tt 025C 1v80.lib
                // // to invoke flat synthesis after netlist generation
>> flatten
// netlist generation
>> show // vew graphical
>> write_verilog therm.v // write the generated netlist to a new module/verilog file
for verification
>> write verilog -noattr therm.v // // to write verilog netlist without
attributes(clean)
Optimize:
>> flatten
>> opt clean -purge
                   // running optimization
>> show
>> write_spice therm.spice
>> show -prefix therm -format svg//save diagram in .svg
>> show -prefix therm -format dot//save diagram in .dot
>> show -enum -prefix therm -format dot //save diagram in .dot with gate numbers
```

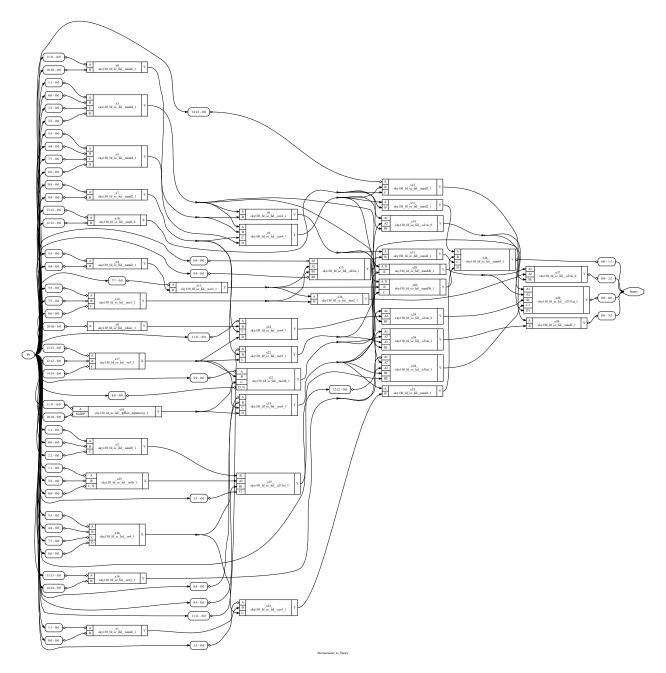

Netlist to schematic conversion:

https://github.com/aidangoettsch/asg

install NetlistViewer:

https://github.com/f18m/netlist-

viewer/blob/master/NetlistViewer/build/linux/README.md

doteditor:

https://sourceforge.net/projects/netlistviewer/

Iverilog with gtkwave:

https://youtu.be/Ryt1ms8Tido


Digital flow with qflow:

http://opencircuitdesign.com/qflow/tutorial nogui.html

Layout editor

https://www.youtube.com/watch?v=K-_6-GMwmc4

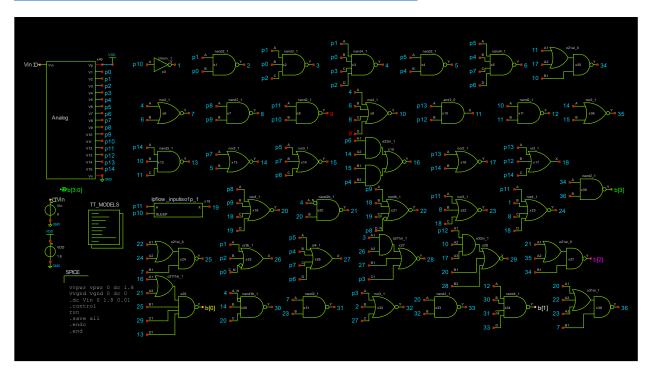https://www.layouteditor.org/layout/basics/installation



Even though Yosys is a useful tool is useful for synthesis, still it is not enough for layout digital logic. It can generate the Verilog netlist and schematic netlist, but to implement the above logic gates either it can be done manually with Magic VLSI (which would be time-consuming, stressful, and prone to error), or using some automation tools flow (ALIGN, qflow, or OpenLane). ALIGN is suitable for analog design, and qflow and OpenLane have already Yosys integrated. For this project I preferred OpenLane. Using qflow or OpenLane the above diagram is not necessary, this steps are already taken care of in the processes. However, the above schematic is still beneficial to compare the prelayout and post-layout results.


OpenLane Procedures:

Install OpenLane- https://github.com/The-OpenROAD-Project/OpenLane

Add a new design in the designs folder:
./flow.tcl -design ADC -init_design_config -add_to_designs

By default it will create config.json file

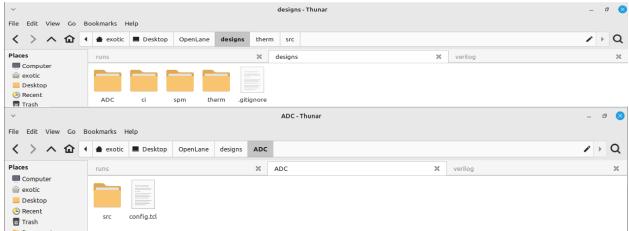If config.ctl is preferred the following command is to be entered:
./flow.tcl -design ADC -init_design_config -add_to_designs -config_file
config.tcl



Now the config.ctl has to be configured accordingly (resolving the errors) and the verilog file need to be copied to src folder, the verilog file name should be same as the design name, otherwise specified in the command.

At first let's try run the processes with default config:

```
./flow.tcl -design ADC
```

Here I have used the verilog code without any clock and I have errors.

```
[WARNING]: PNR SDC FILE is not set. It is recommended to write a custom SDC file for the design. Defaulting to BASE_SDC_FILE
[WARNING]: SIGNOFF_SDC_FILE is not set. It is recommended to write a custom SDC file for the design. Defaulting to BASE_SDC_FILE
[INFO]: Running linter (Verilator) (log: designs/ADC/runs/RUN_2023.12.26_11.29.39/logs/synthesis/linter.log)...

ERROR[: 2 errors found by linter

ERROR[: Step 0 (verilator lint check) failed with error:
code 1 -level 0 -errorcode NONE -errorinfo {
    while executing

"throw error"
    (procedure "run verilator" line 86)
    invoked from within

run verilator"
    (procedure "run verilator_step" line 3)
    invoked from within

"run verilator_step"} -errorline 1
```

Lets have look at the log file named linter.log

```
# therm.v x spm.v x pin_order.cfg x config.td x linter.log x

# Error: Specified --top-module 'ADC' was not found in design.

# Error: Exiting due to 1 error(s)
```

As the design/file name is ADC, but the module name in the code is different, it throwed the erros. I have changed the module name to ADC, and lets run it again.

```
[ERROR PDN-0175] Pitch 5.9800 is too small for, must be atleast 6.6000
Error: pdn_cfg.tcl, 92 PDN-0175
child process exited abnormally
```

Now there is Pitch error. Let's edit config.tcl file, adding the following lines:

```
set ::env(FP_PDN_AUTO_ADJUST) 0
set ::env(FP_PDN_VPITCH) 7.0
set ::env(FP_PDN_VOFFSET) 7.0
```


after adding above lines the error is gone but new error appeared.


```
[ERROR]: during executing openroad script /openlame/scripts/openroad/gpl.tcl
[ERROR]: Log: designs/ADC/runs/RUN_2023.12.26_14.25.51/logs/placement/6-global_skip_io.log
[ERROR]: Last 10 lines:
[INFO GPL-0017] MonPlaceInstsArea: 66313600
[INFO GPL-0018] PlaceInstsArea: 294032000
[INFO GPL-0019] Util(%): 64.74
[INFO GPL-0020] StdInstsArea: 294032000
[INFO GPL-0021] MacroInstsArea: 0
[ERROR GPL-0302] Use a higher -density or re-floorplan with a larger core area.
[ivem target density: 0.60
[suggested target density: 0.65
[tror: gpl.tcl, 75 GPL-0302]
[child process exited abnormally
[ERROR]: Creating issue reproducible...
```

Adding another line to fix that error:

set ::env(PL_TARGET_DENSITY) "0.65"

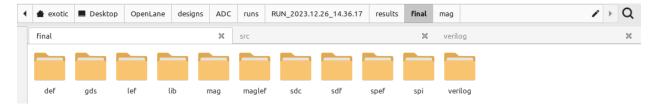now the layout has generated in different formats.



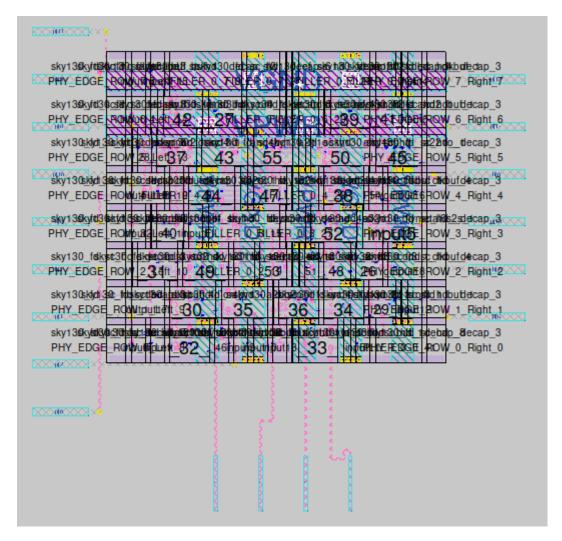

It is the digital part of the layout. For the analog part I preferred ALIGN.

Install ALIGN VLSI:

https://github.com/ALIGN-analoglayout/ALIGN-puhttps://github.com/syedimaduddin/msvsd4bituc/tree/main/Week-2blic

Run ALIGN:

```
python3 -m venv general
source general/bin/activate
schematic2layout.py ../ADC/Analog -p ../pdks/SKY130_PDK/
```


- simulate the complete (ultra small) ADC

Prelayout simulation:

To run these standard cells the "TT_MODELS" content should be:

,,,

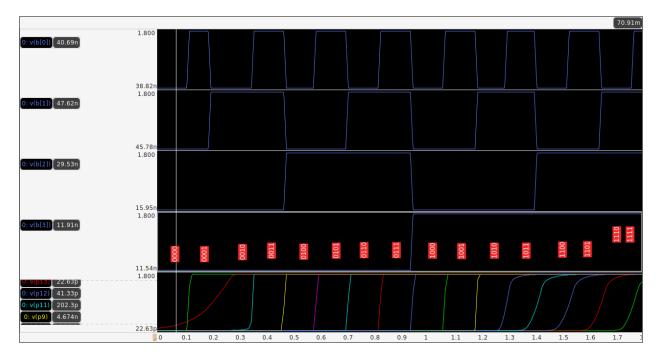name=TT_MODELS
only_toplevel=true
format="tclevel(@value)"
value=".lib \$::SKYWATER_MODELS/sky130.lib.spice tt
.include \$::SKYWATER_STDCELLS/sky130_fd_sc_hd.spice"
Spice_ignore=false



References:

https://github.com/bluecmd/learn-sky130/blob/main/schematic/xschem/getting-started.md

OpenLane:

https://openlane.readthedocs.io/en/latest/usage/exploration_script.html

Magic VLSI command/long commands

check channel before or after routing

:channel

Clear the channel/any feedback view

:feedback clear

Open netlist window


:specialopen netlist


Save netlist (save and autowrite)

extract do local
extract all
ext2spice lvs
ext2spice cthresh 0 rthresh 0
ext2spice


Analog Design:


Th. 15 (1.782)

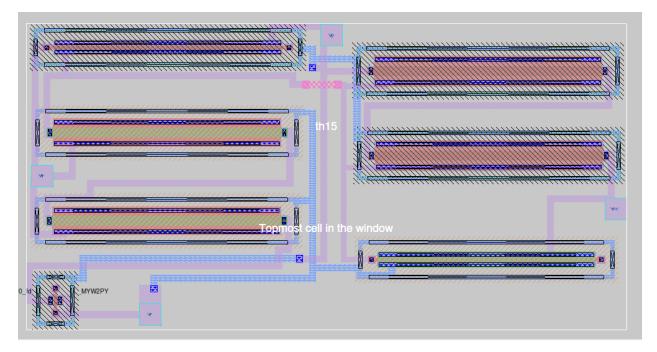

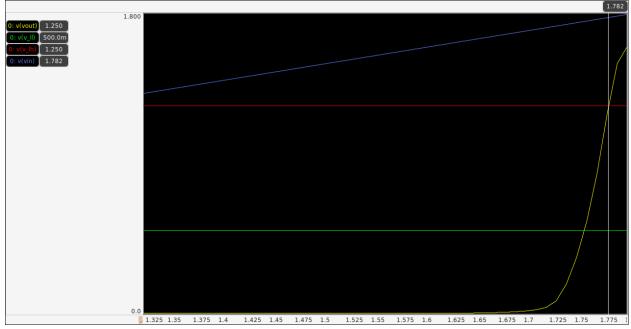



Th. 14 (1.663)

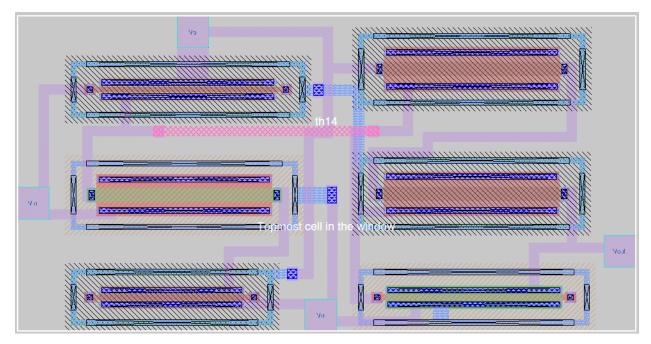

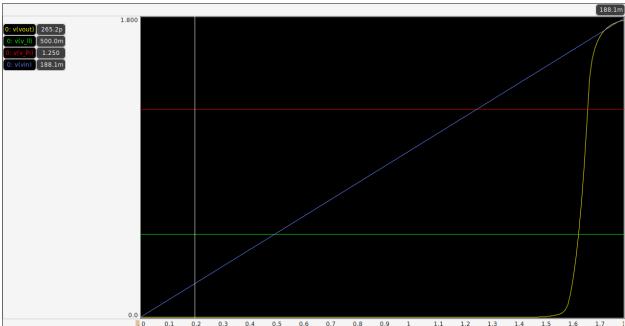



Th. 13 (1.544)

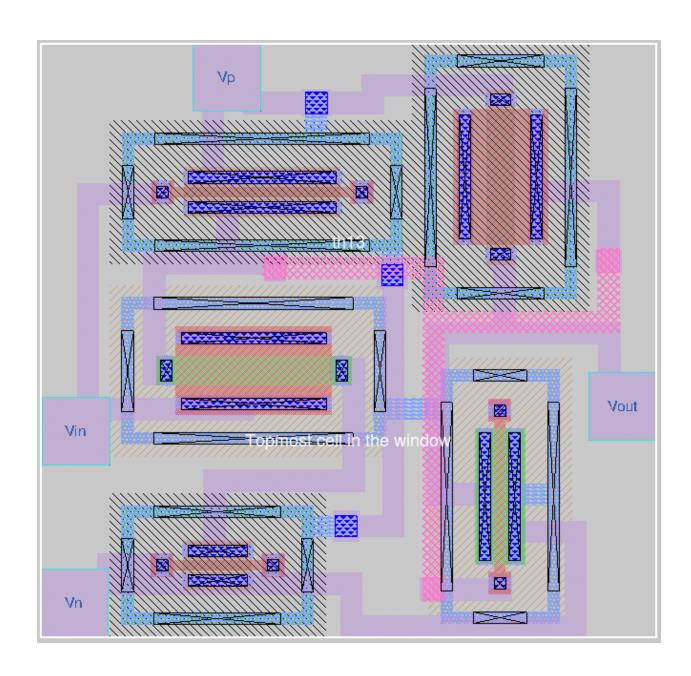

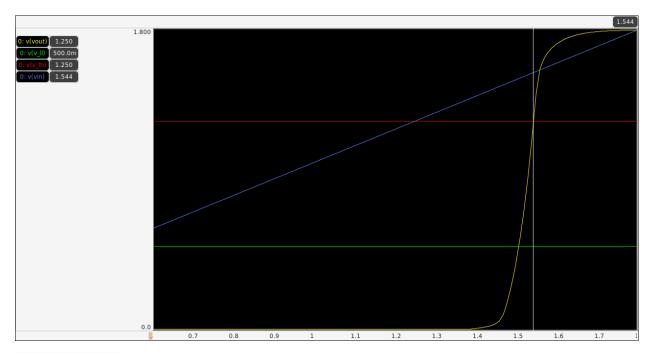



Th. 12 (1.419)

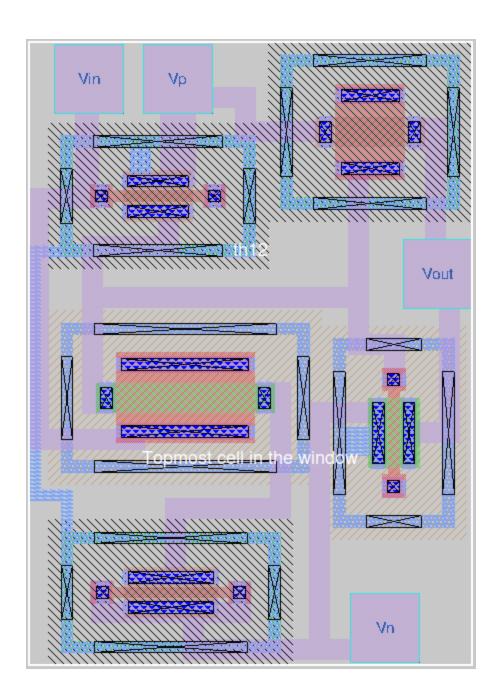

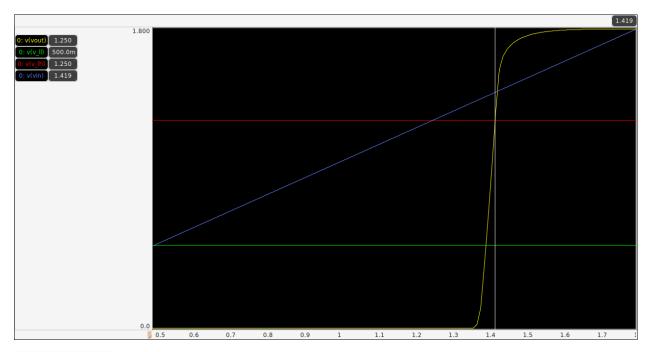



Th. 11 (1.30)

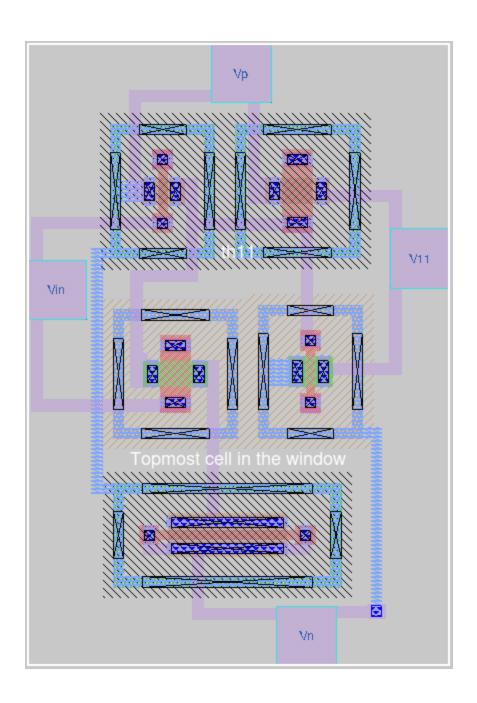

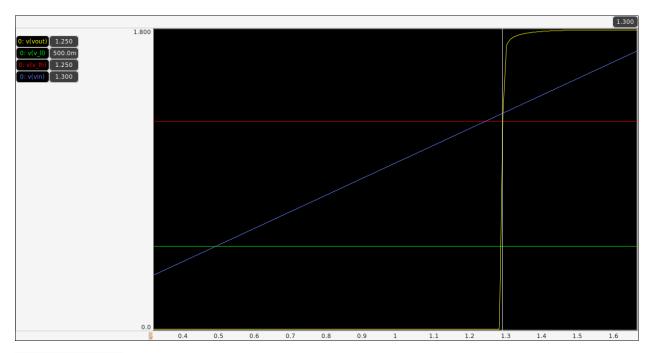



Th. 10 (1.198)

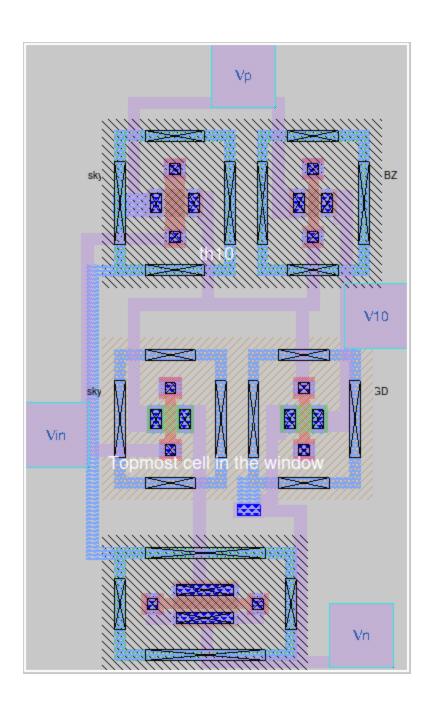

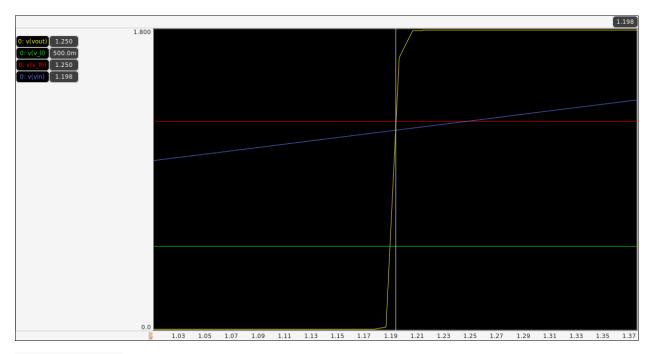



Th. 09 (1.057)

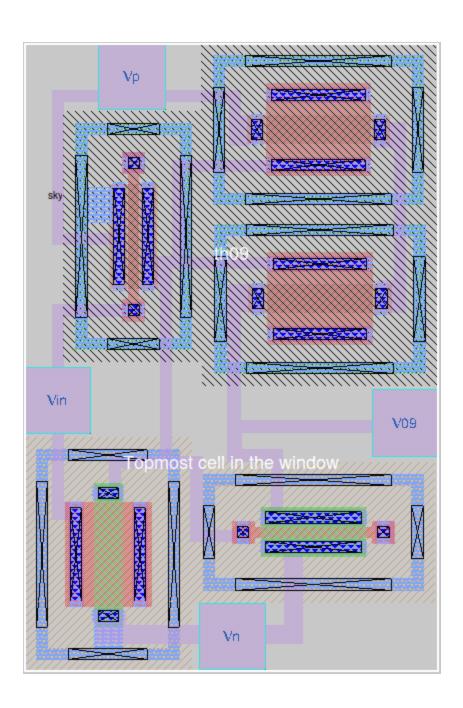

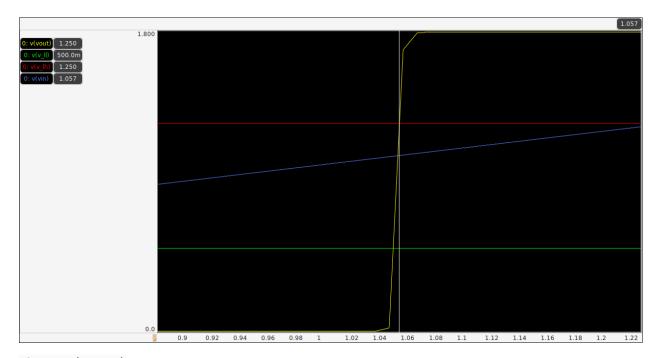



Th. 08 (0.937)

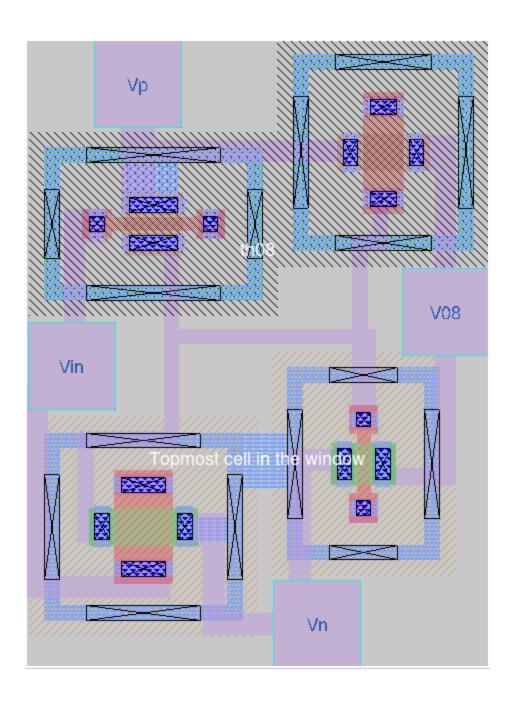

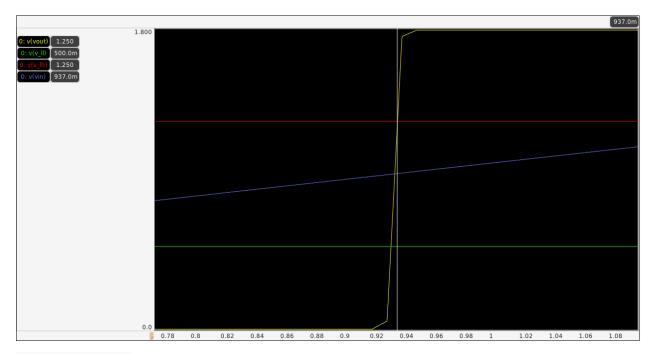



Th. 07 (0.8375)

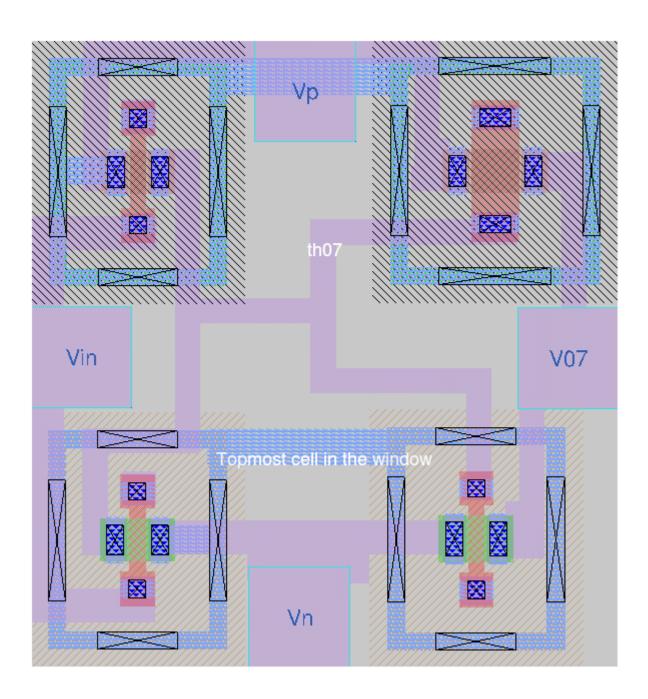

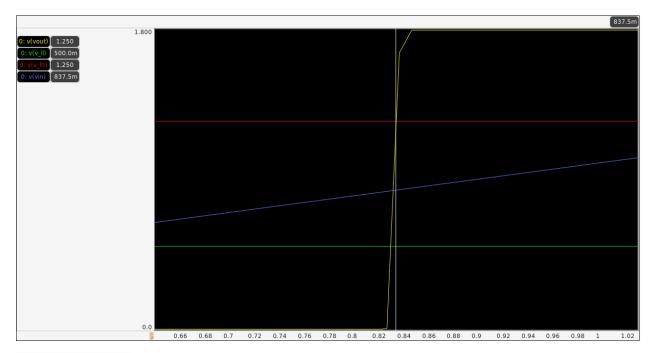



Th. 06 (0.7278)

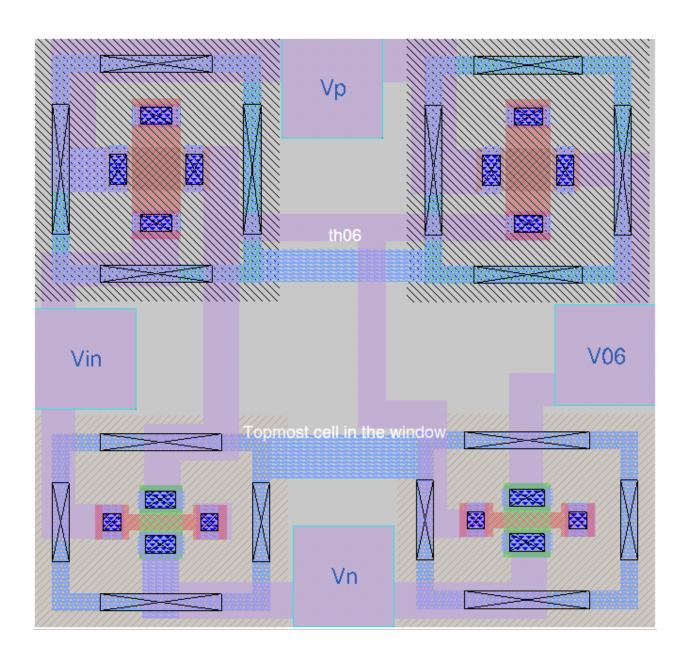

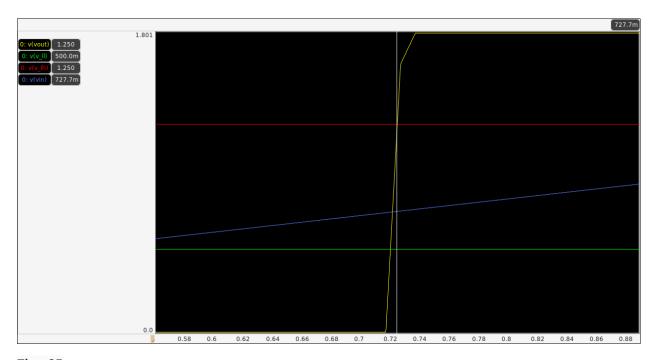



Th. 05

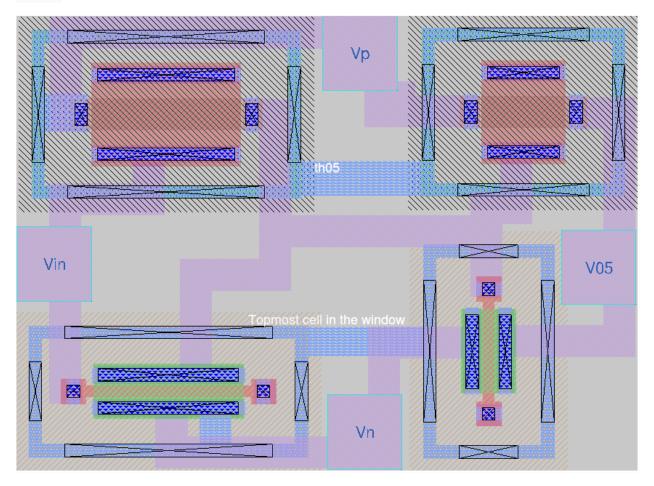

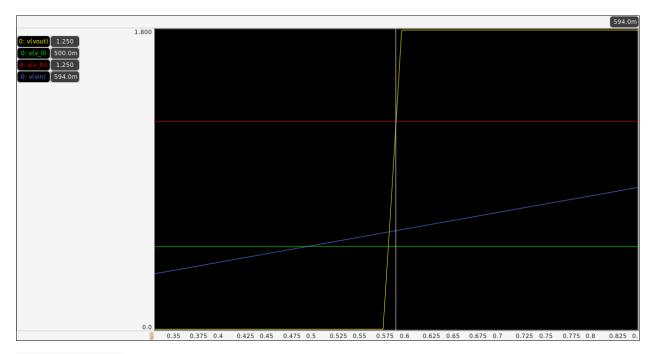



Th. 04 (0.487)

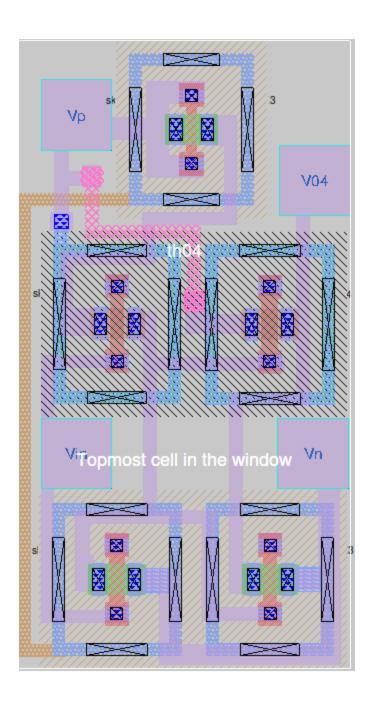

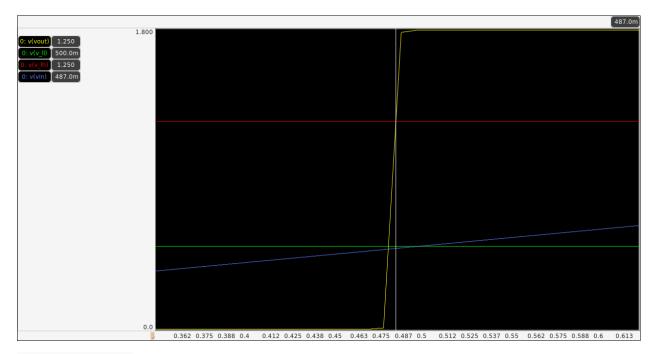


Th. 03 (0.3667)

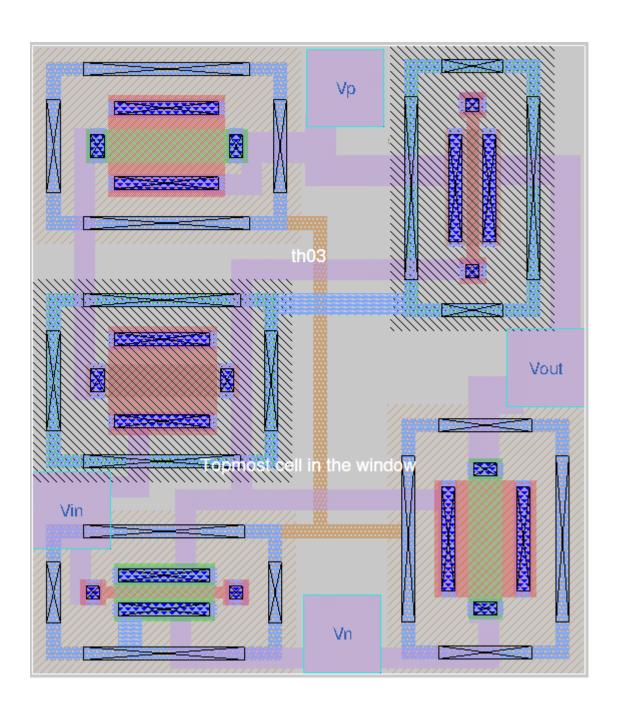


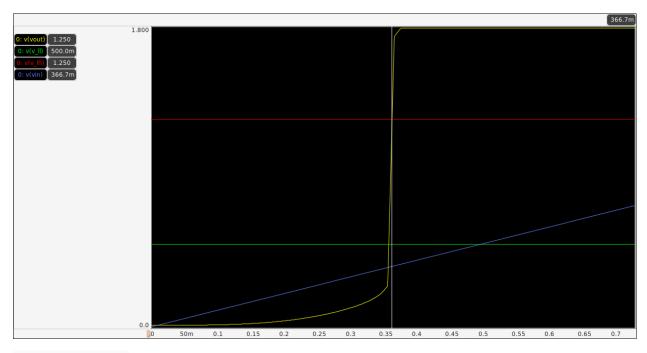


Th. 02 (0.2156)

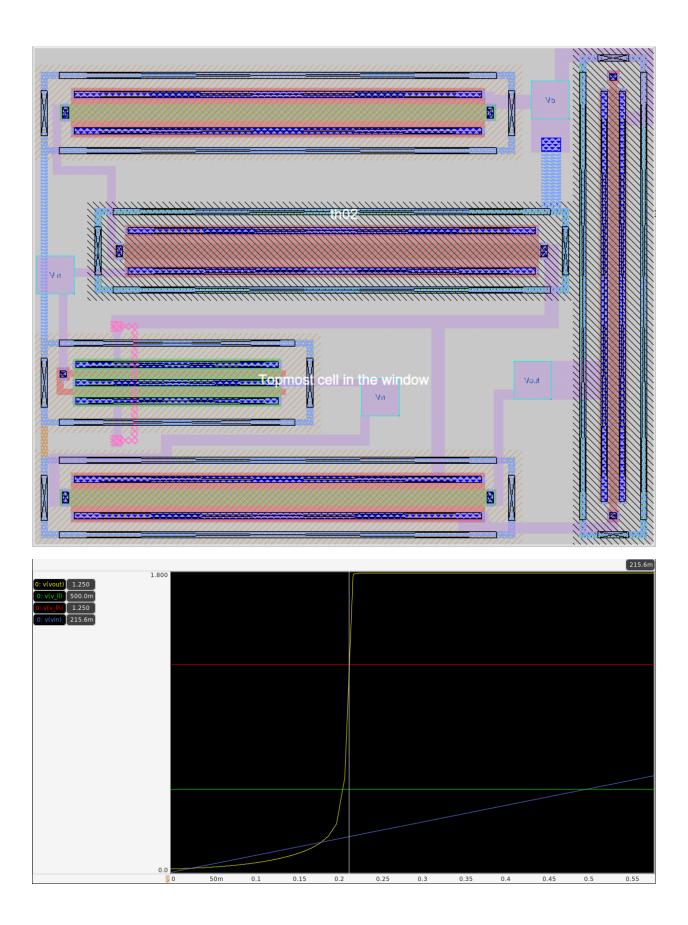



Th. 01 (0.1182)

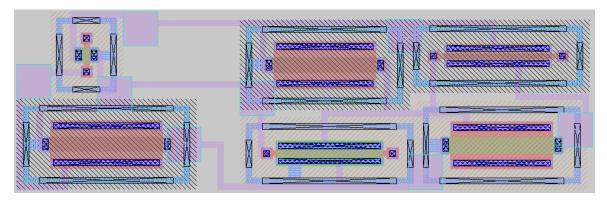

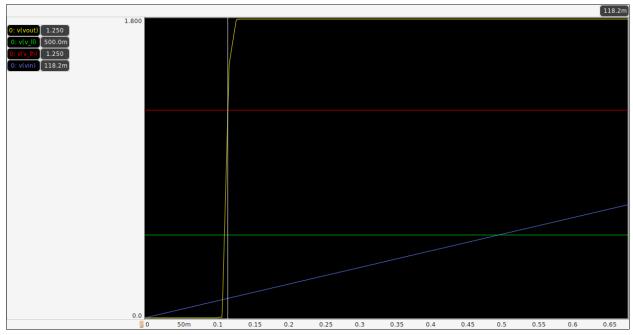

Combined Layout:

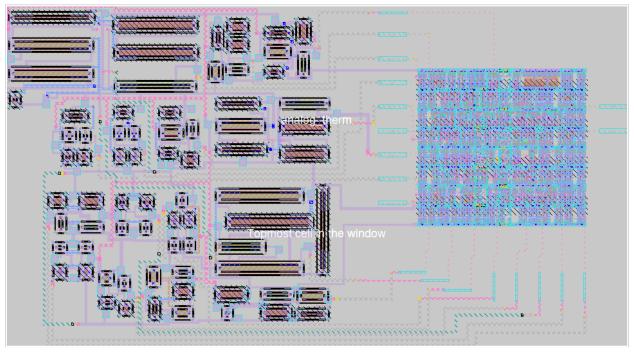

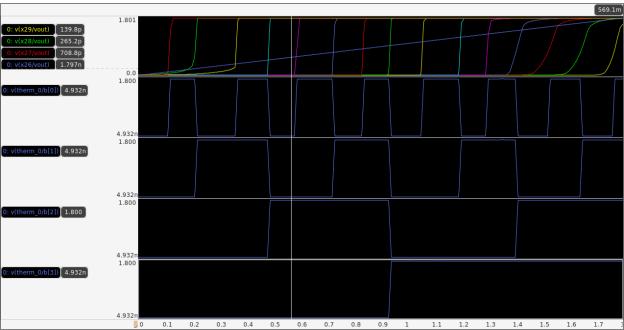

Run iverilo/icarus

iverilog file.v

vvp a.out

