

Topic of the project:

Project name: "ASIC design with open source tools"

Developing of an low resolution ADC. As example an 4-Bit ADC with conversion of the thermometer code into binary code.


Steps:

A small CMOS inverter with xschem and the sky130a technology (PDK)  
and simulate the circuit with ngspice:


**Binary Logic level assumption**

[https://en.wikipedia.org/wiki/Logic\\_level](https://en.wikipedia.org/wiki/Logic_level)

Technology	L Voltage	H Voltage	note
CMOS	0 to 30% of Vdd	70% of Vdd to Vdd	Vdd = Supply voltage
	≈0.5 Volt	≈1.25 Volts	Vdd = 1.8 Volts

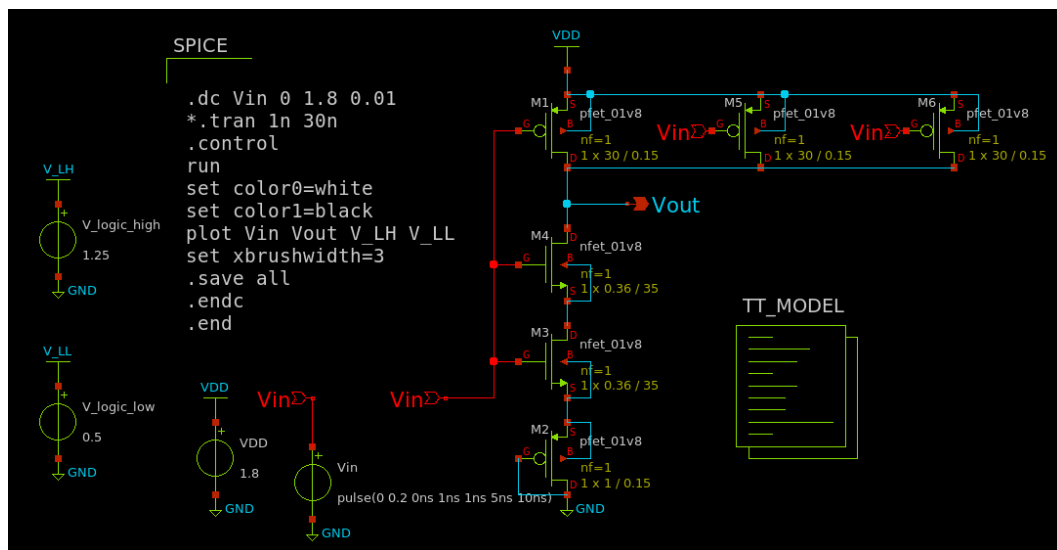

 The above figure is the schematic for 15<sup>th</sup> threshold point of the analogue part of the ADC.  
The plot is as follows:




The inverter will switch from logic-high or undefined to logic-zero when input voltage exceeds 1.68 volts. So, for this inverter the threshold is 1.68 volts.

For a 4-bit ADC we need 16 voltage level including zero (0~1.68 volts). The quantization should be  $1.68/16=0.112$  volts.

**Vdd = 1.8 V**

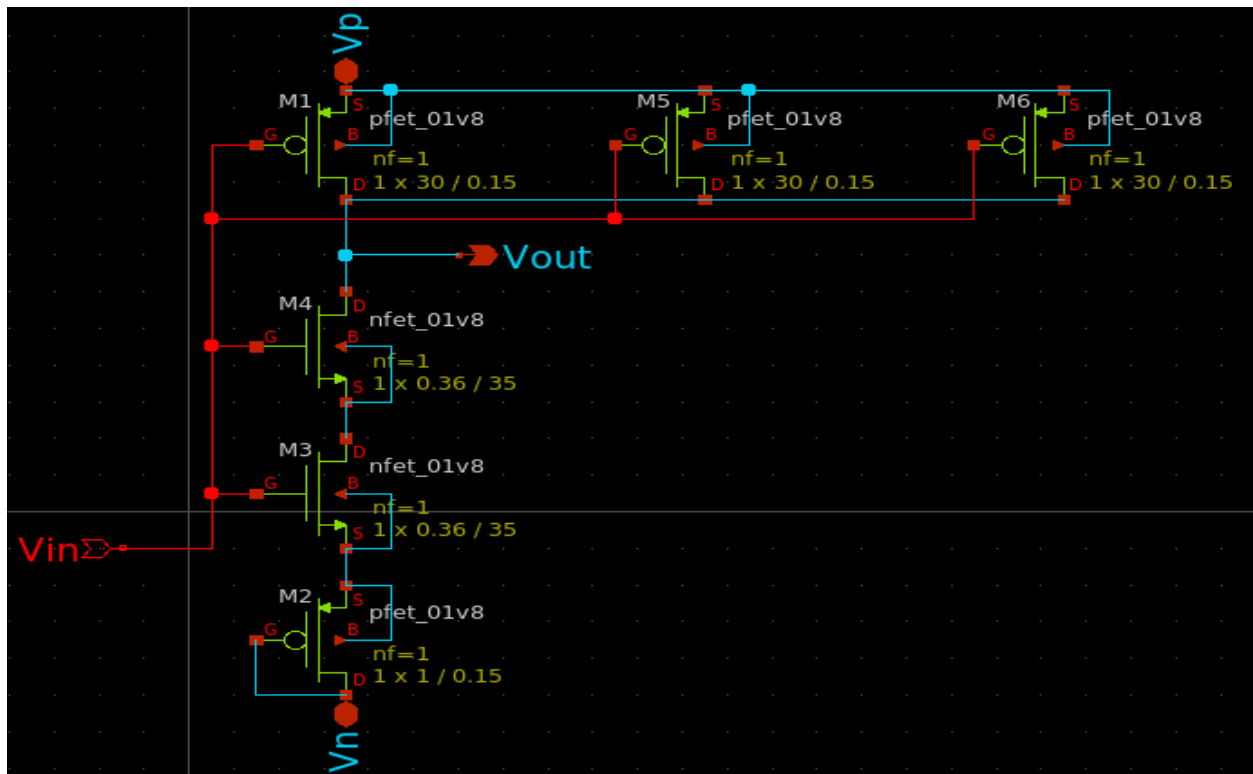**Th. 15: 1.680**

For calculation the schematic and the plot already mentioned earlier. Remove all source to make symbol from schematic. As the symbol will have to be connected to Vdd and GND, those pins are replaced with Vp and Vn accordingly.




File Edit Options View Properties **Layers** Tools Symbol Highlight Simulation

Inverter-th15\_sym.sch Inverter-th15\_sym.sch


- Show symbols Alt+B
- Show instance Bounding boxes for subcircuit symbols Alt+B
- Show instance Bounding boxes for all symbols Alt+B
- Show net names on symbol pins/floater
- Set symbol width
- Make symbol from schematic A
- Make schematic from symbol Ctrl+L
- Make schematic and symbol from selected components Ctrl+Shift+H
- Attach net labels to component instance Shift+H
- Create symbol pins from selected schematic pins Alt+H
- Place symbol pin Alt+P
- Print list of highlight nets J
- Print list of highlight nets, with buses expanded Alt-Ctrl-J
- Create labels from highlight nets Alt-J
- Create labels from highlight nets with 'i' prefix Alt-Shift-J
- Create pins from highlight nets Ctrl-J
- Search all search-paths for schematic associated to symbol
- Allow duplicated instance names (refdes)



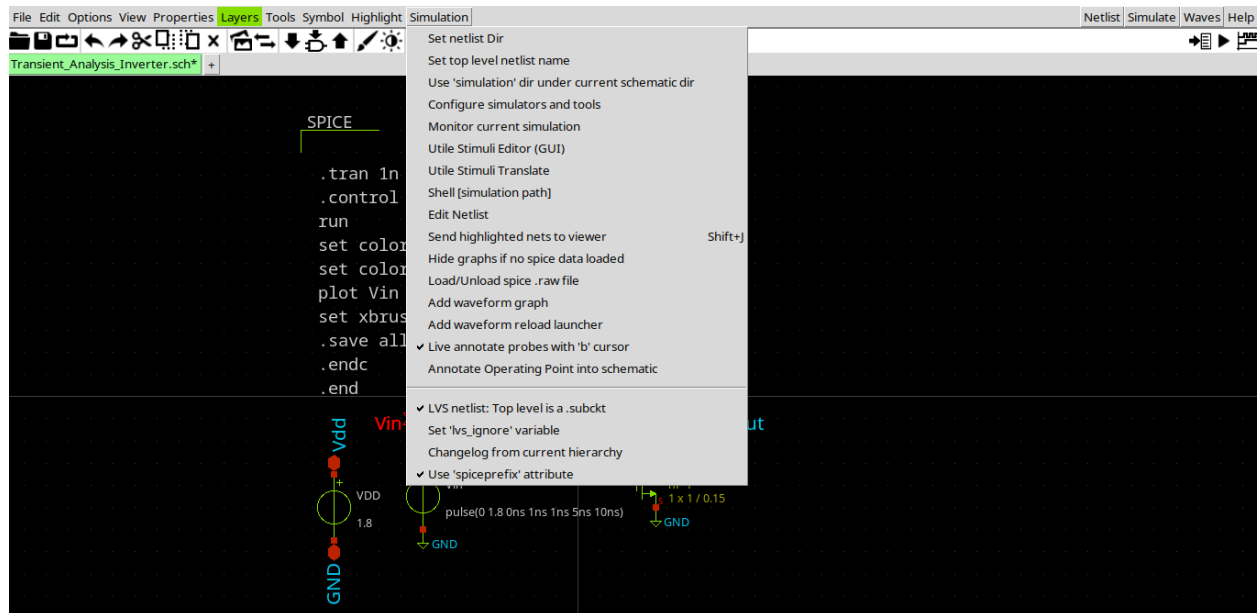Magic=>before importing netlist to ngspice check LVS net





The simplified schematic is as follows:

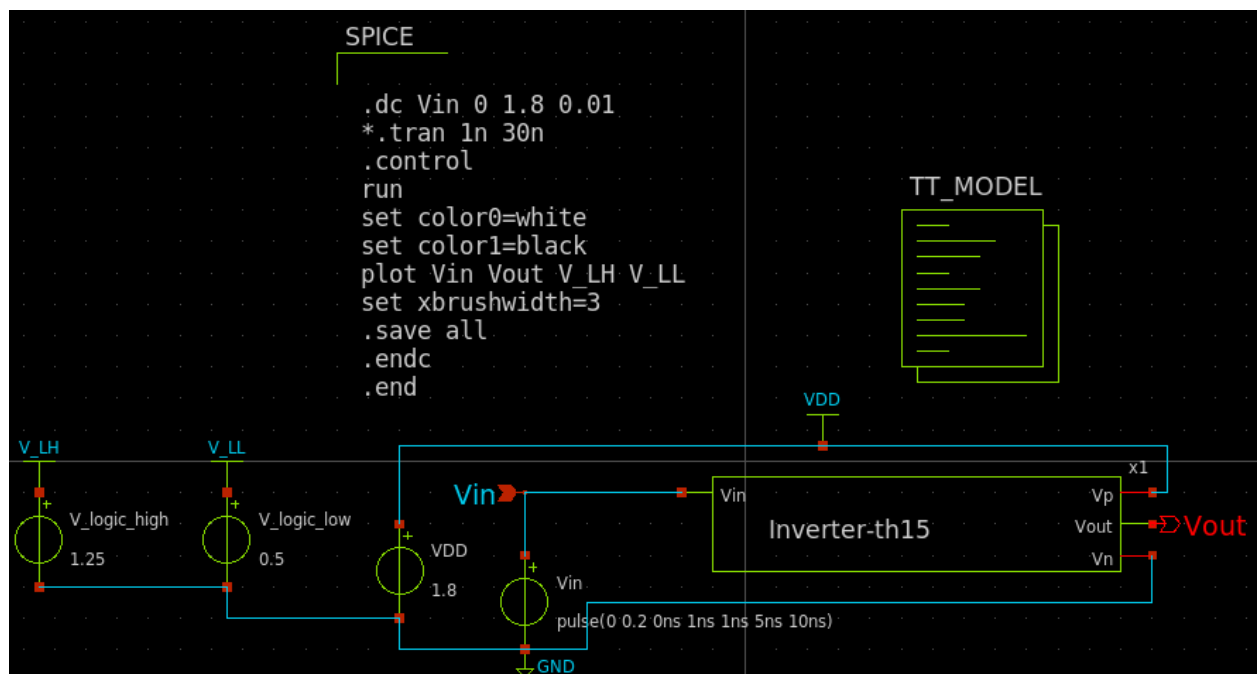



The plot is similar to the previous figure.

**Th. 14: 1.568**

 
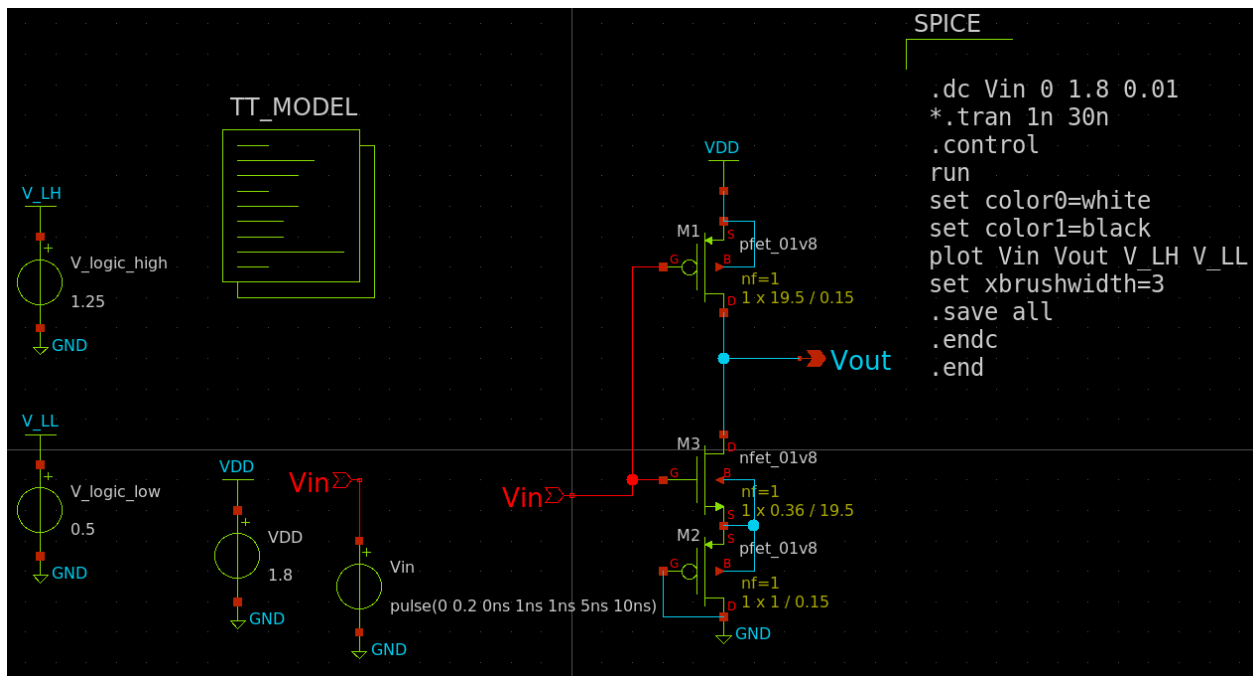


Rest of the figures are similar to the previous figures.



**Th. 13: 1.456:**

 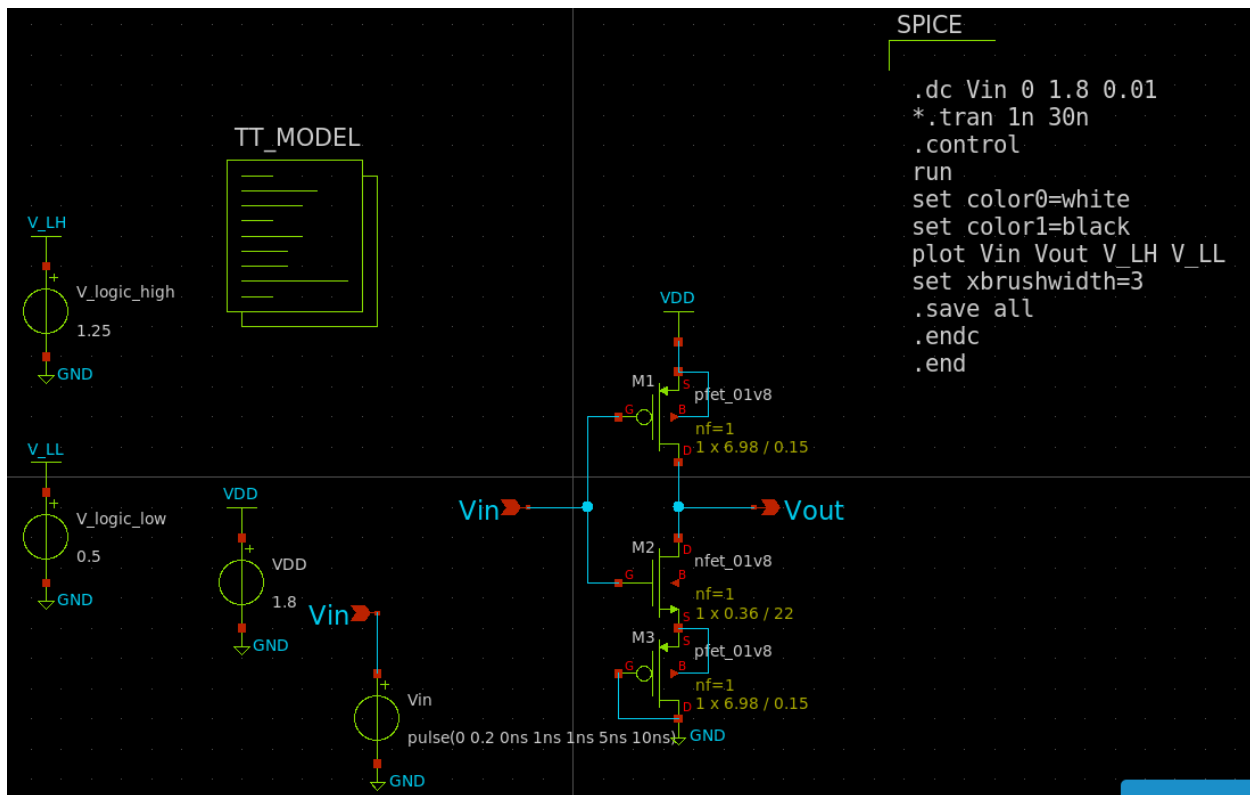

Th. 12: 1.344

 
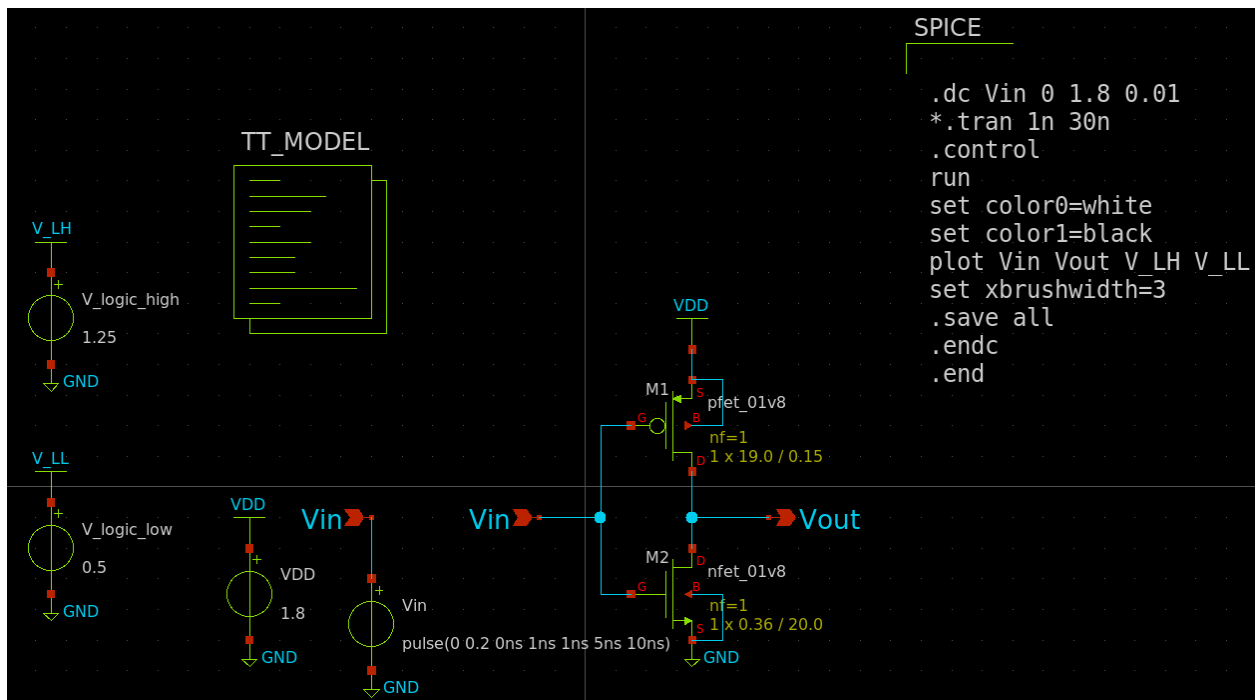


Th. 11: 1.232

 
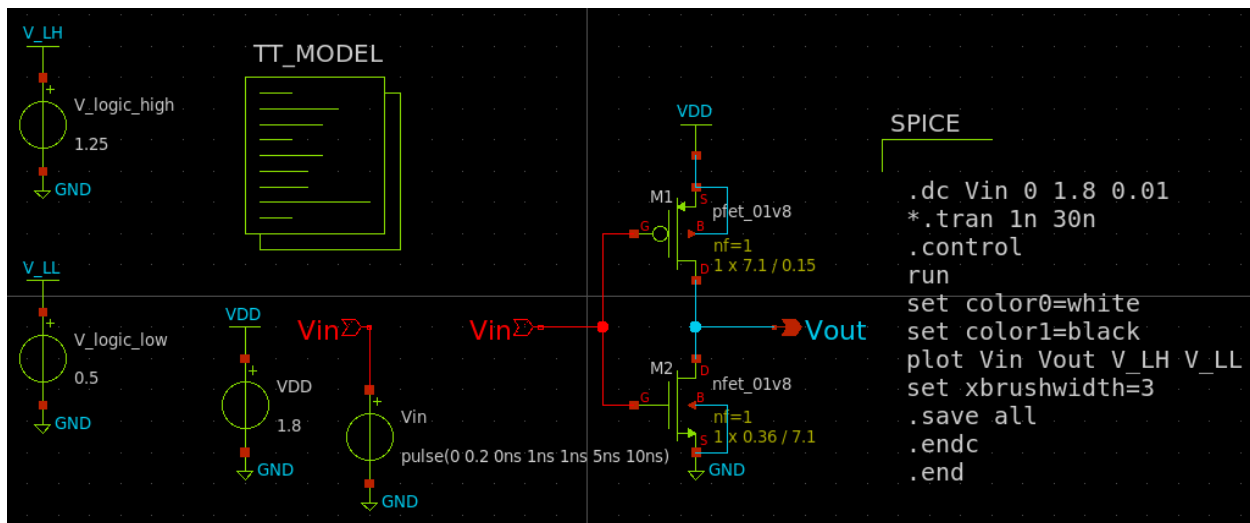


Th. 10: 1.12




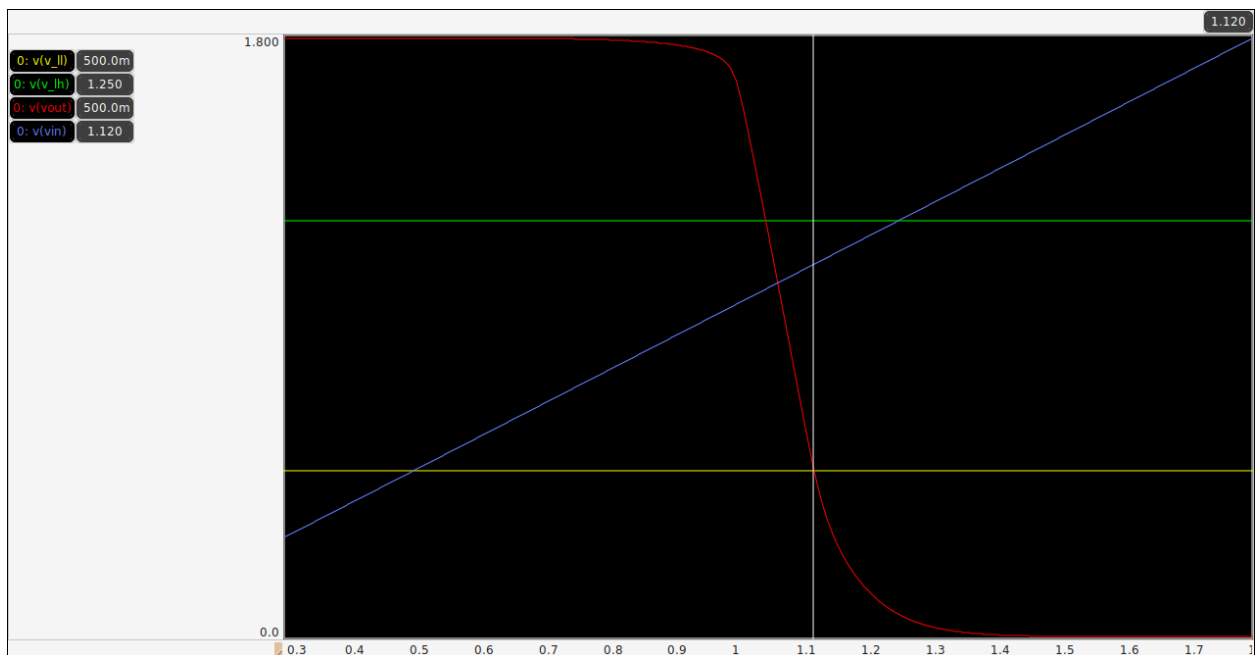 


Th. 9: 1.008

 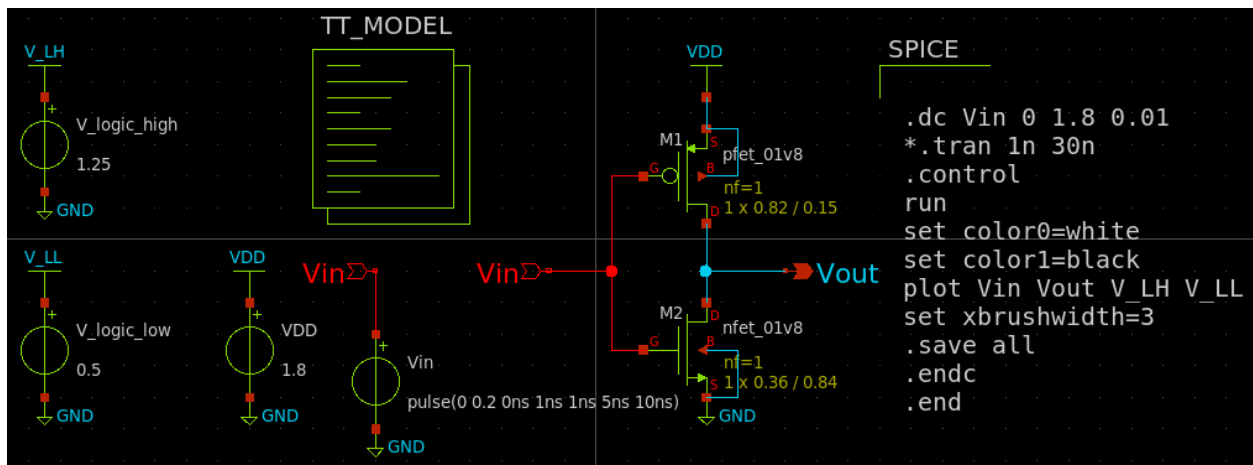



Th. 8: 0.896

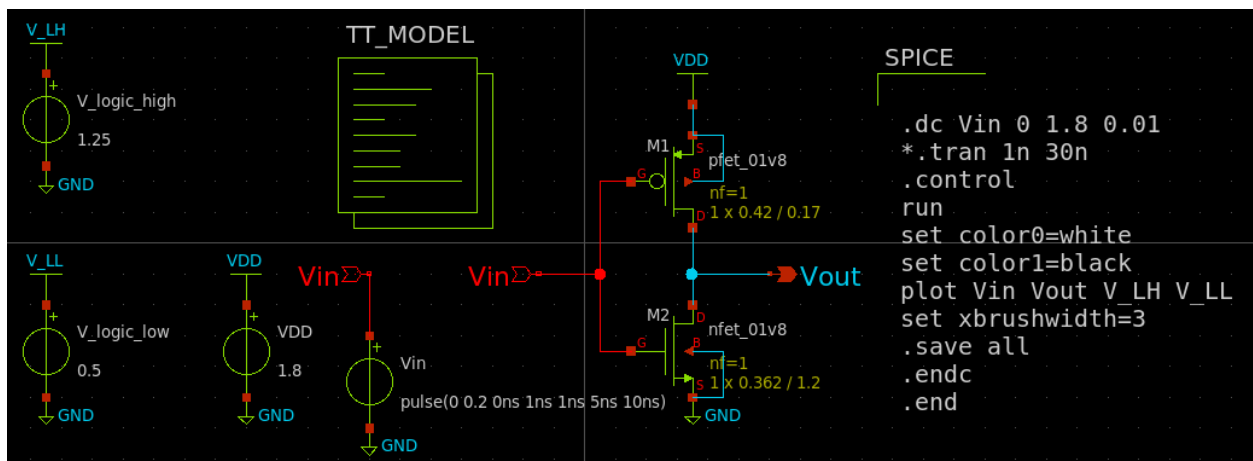

 



Th. 7: 0.784

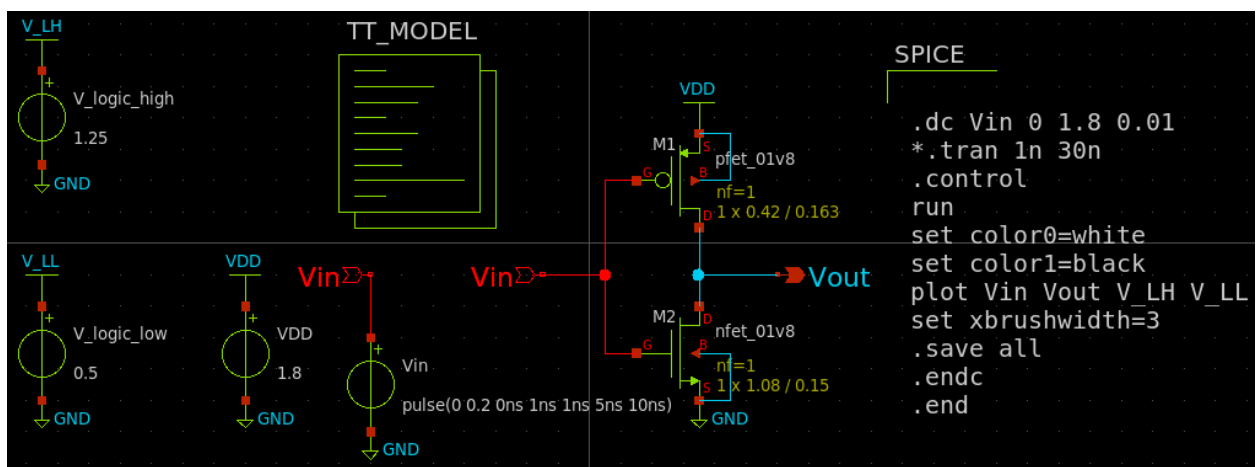

 



Th. 6: 0.672

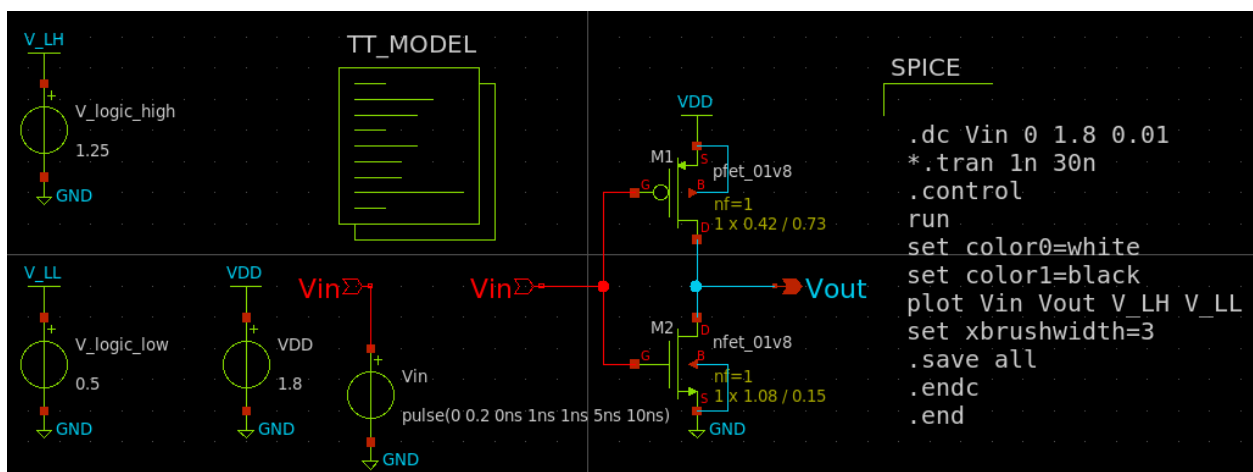

 



Th. 5: 0.56

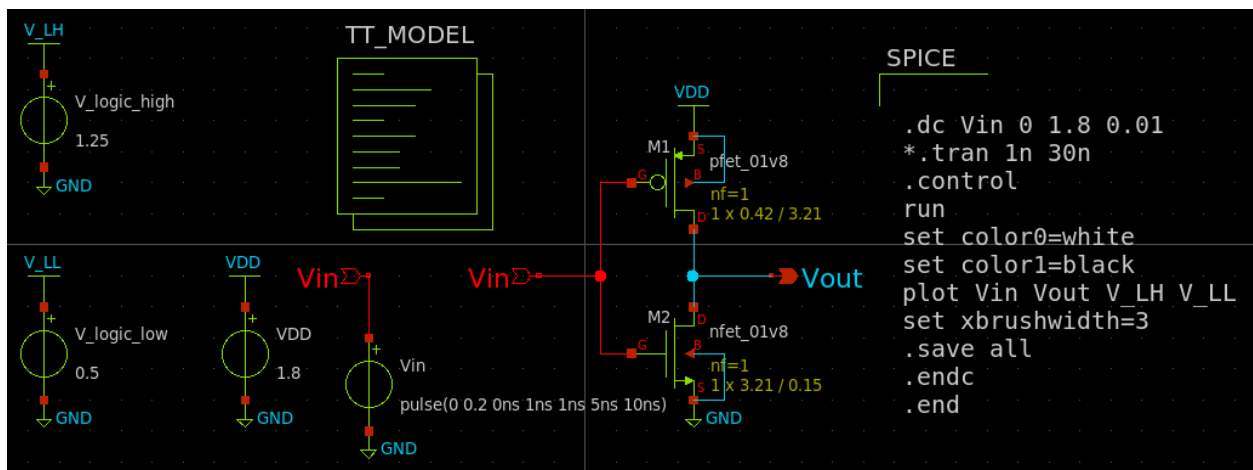

 



Th. 4: 0.448

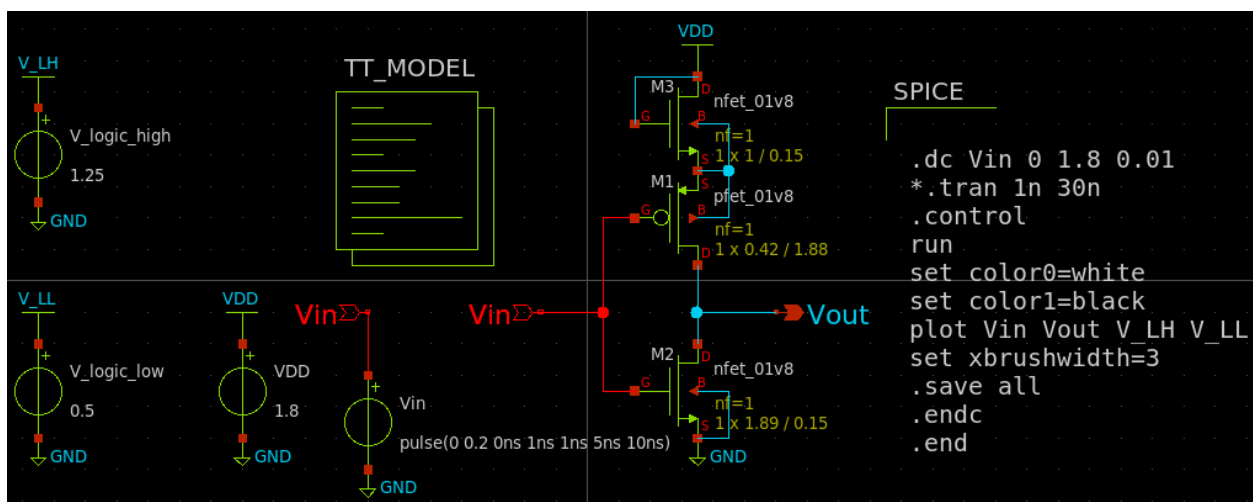

 


Th. 3: 0.336

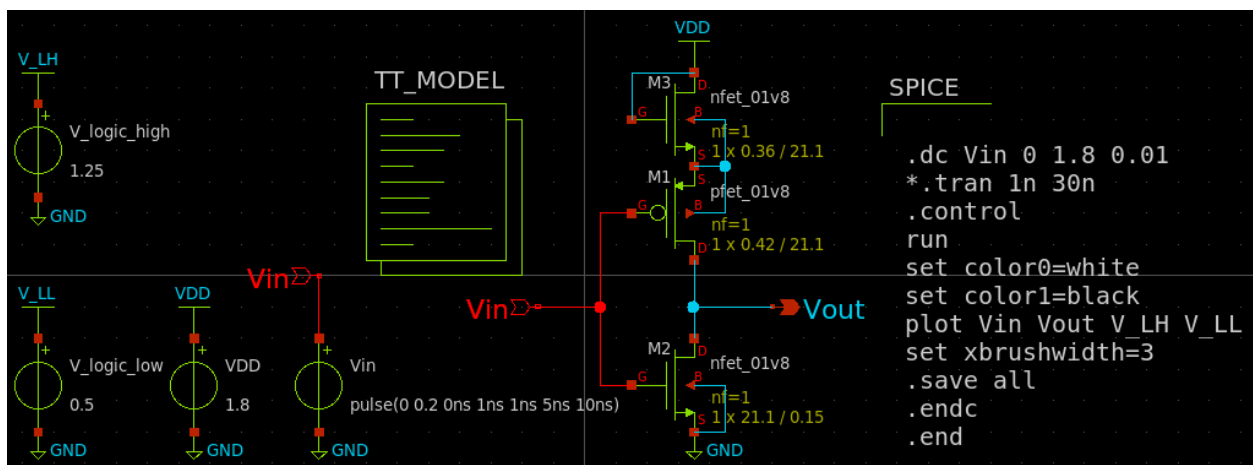


 


Th. 2: 0.224

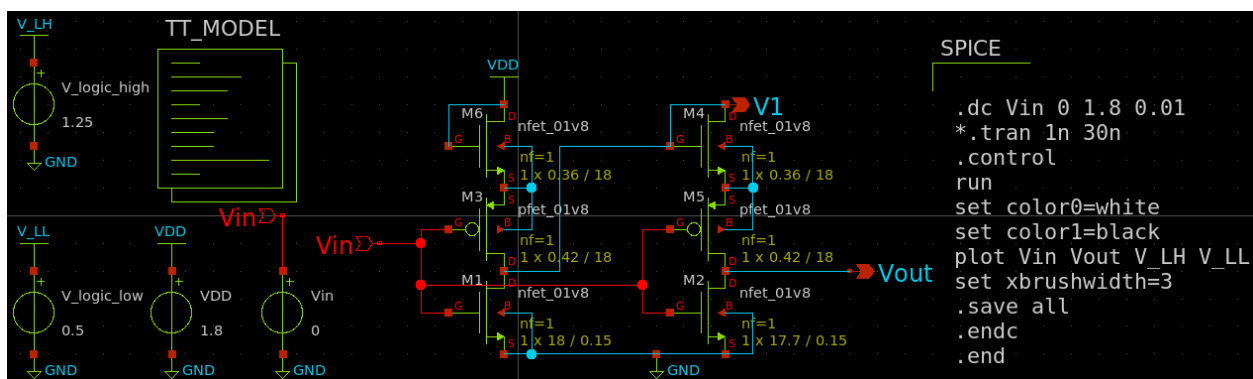




 



Th. 1: 0.112

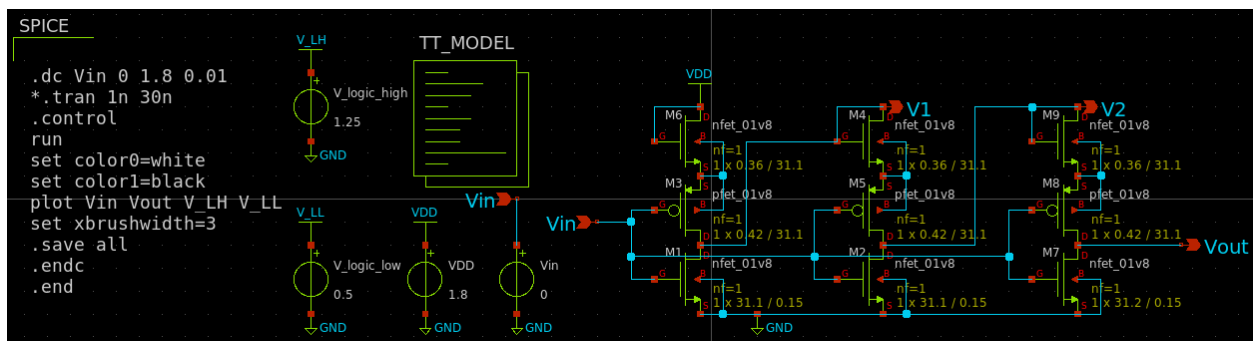

 

## Combined Analog sch.

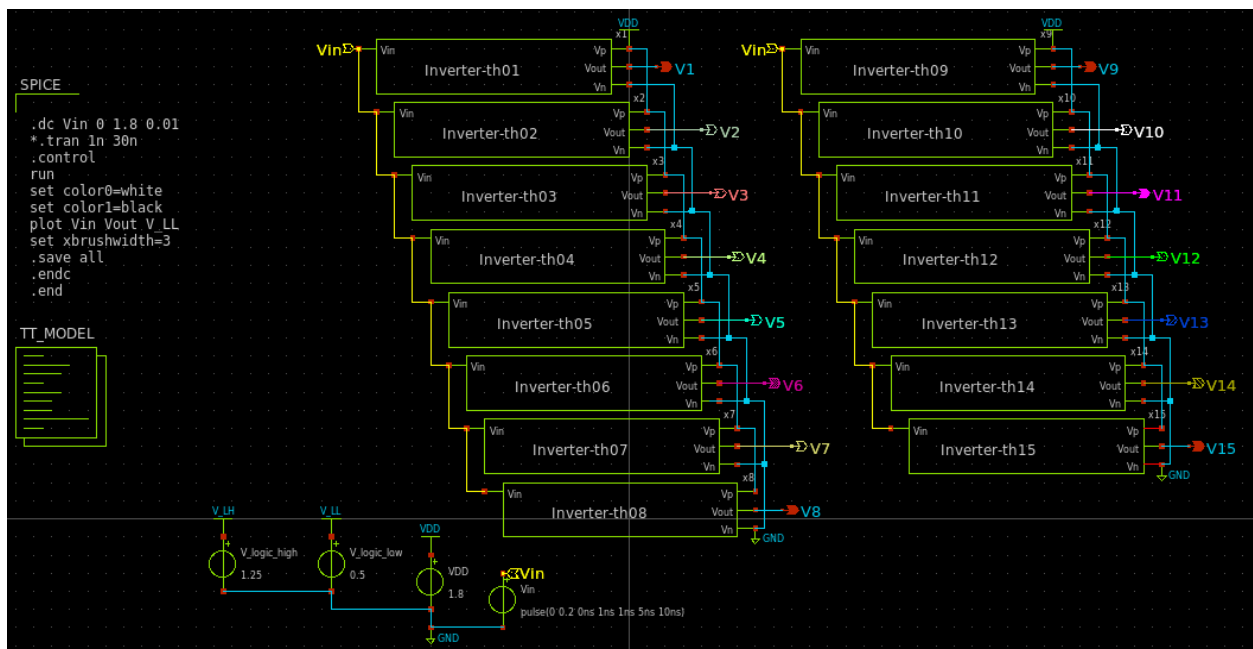

 

<http://web02.gonzaga.edu/faculty/talarico/vlsi/xschemTut.html>

<https://ngspice.sourceforge.io/ngspice-control-language-tutorial.html>

### **Alter subckt tutorial—**

<https://sourceforge.net/p/ngspice/discussion/133842/thread/5ad086c79f>

<https://sourceforge.net/p/ngspice/discussion/133842/thread/9a75acf2/#bf90/45b3/ea48>

### **Pyspice ngspice interpreter**

<https://pyspice.fabrice-salvaire.fr/releases/v1.3/examples/ngspice-shared/ngspice-interpreter.html>

<https://github.com/ashwith/ngspicepy>

### **Read spice raw output data**

<https://gist.github.com/snmishra/27dcc624b639c2626137/raw/742fe0dd59c7b2c41b71a1c8c1c2506d13affc53/rawread.py>

## ngspice wrapper for python

<https://github.com/eps82/lyngspice/wiki>

write some verilog code to convert the thermometer code (from the inverter stages) into the binary code

<http://www.asic-world.com/verilog/veritut.html>

<https://nandland.com/introduction-to-verilog-for-beginners-with-code-examples/>

[https://www.youtube.com/playlist?list=PLfGJELQIDBN0VsXQ68\\_FEYyqcym8CTDN](https://www.youtube.com/playlist?list=PLfGJELQIDBN0VsXQ68_FEYyqcym8CTDN)

<https://github.com/Swagatika-Meher/msvds2bitcomp>

## ALIGN Tool-

[https://www.youtube.com/playlist?list=PLvXKBnlvcSm30Y0zu1765oG\\_x-ECU8tVG](https://www.youtube.com/playlist?list=PLvXKBnlvcSm30Y0zu1765oG_x-ECU8tVG)

<https://learning.edx.org/course/course-v1:HarveyMuddX+ENGR85A+3T2021/home>

<https://www.vlsiuniverse.com/digital-thermometer-code-in-verilog-vhdl-flash-adc-binary-encoder/>

<https://www.classcentral.com/subject/vlsi?free=true>

<https://www.eng.biu.ac.il/temanad/digital-vlsi-design/>

[https://www.youtube.com/playlist?list=PLZU5hLL\\_713x0\\_AV\\_rVbay0pWmED7992G](https://www.youtube.com/playlist?list=PLZU5hLL_713x0_AV_rVbay0pWmED7992G)

[https://youtu.be/BlqLk23hE90?list=PLZU5hLL\\_713x0\\_AV\\_rVbay0pWmED7992G](https://youtu.be/BlqLk23hE90?list=PLZU5hLL_713x0_AV_rVbay0pWmED7992G)

get familiar with the yosis syntesis tool to convert the verilog code into a CMOS circuit

<https://www.mehmetburakaykenar.com/synthesis-n-bit-counter-with-open-source-yosys-synthesizer/294/>

[https://github.com/spdy1895/RTL\\_synthesis\\_using\\_sky130](https://github.com/spdy1895/RTL_synthesis_using_sky130)

<https://github.com/Imellal/RTL-workshop-Sky130-PDK>


After install YoSys (see the bash file in the repository), run the following commands—

```
>> yosys          // open yosys console in terminal
```


```
>> read_liberty -lib
```

```
/usr/local/share/pdk/sky130A/libs.ref/sky130_fd_sc_hs/lib/sky130_fd_sc_hs__tt_025C_1v89.lib
```

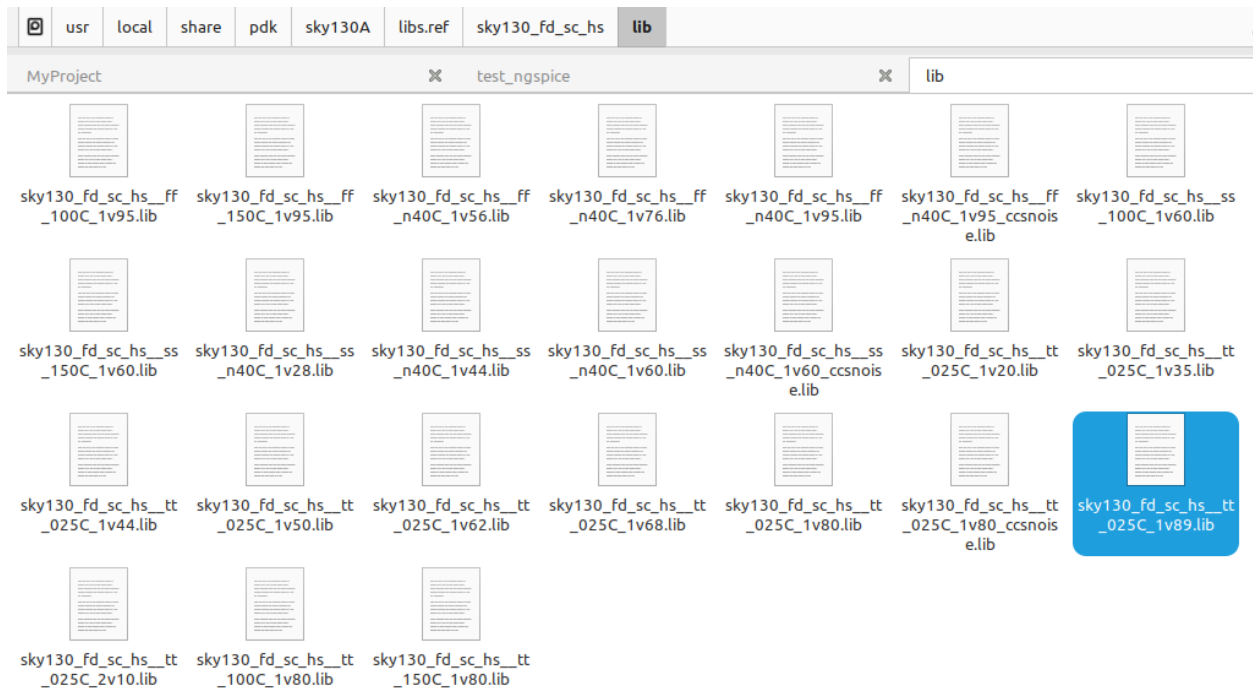// reading the suitable liberty file (see the screenshot below)


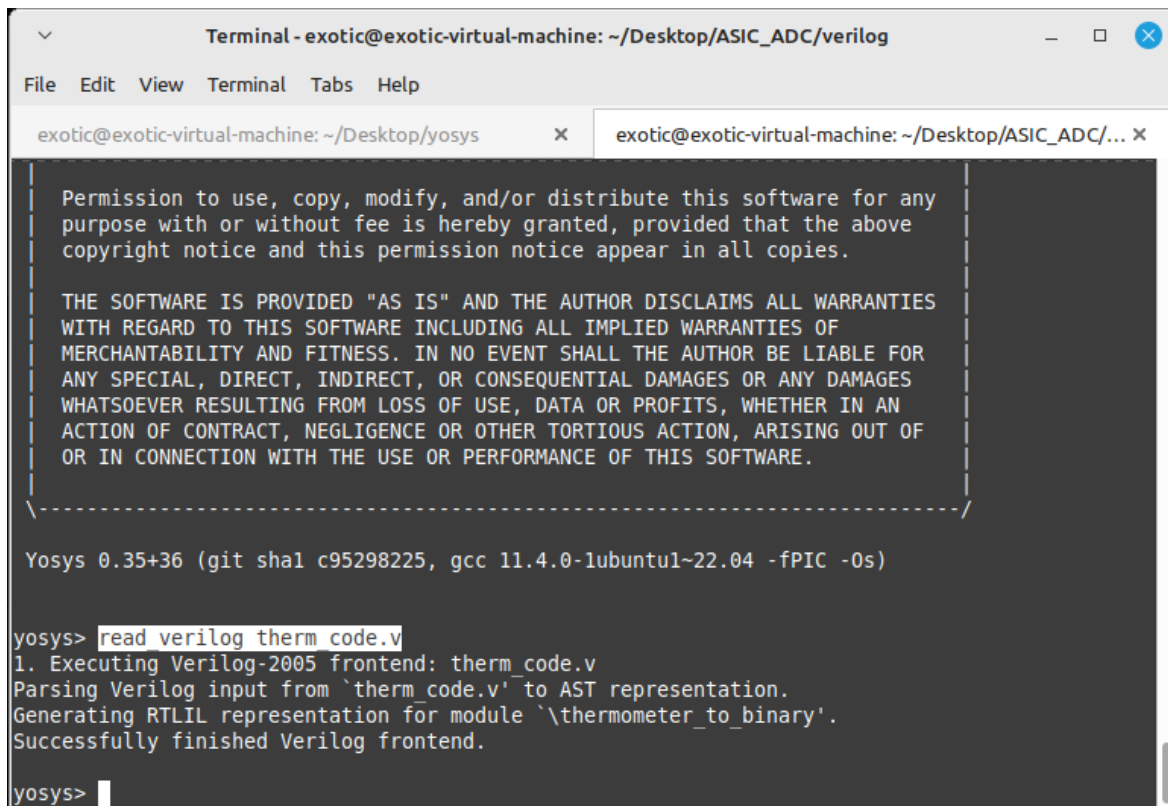
>> read\_verilog therm\_code.v // read the verilog file



>> synth -top thermometer\_to\_binary // synthesize the module


```
>> abc -liberty
```

```
/usr/local/share/pdk/sky130A/libs.ref/sky130_fd_sc_hs/lib/sky130_fd_sc_hs__tt_025C_1v89.lib
```

```
>> flatten // // to invoke flat synthesis after netlist generation
```

```
// netlist generation
```

```
>> show // view graphical
```

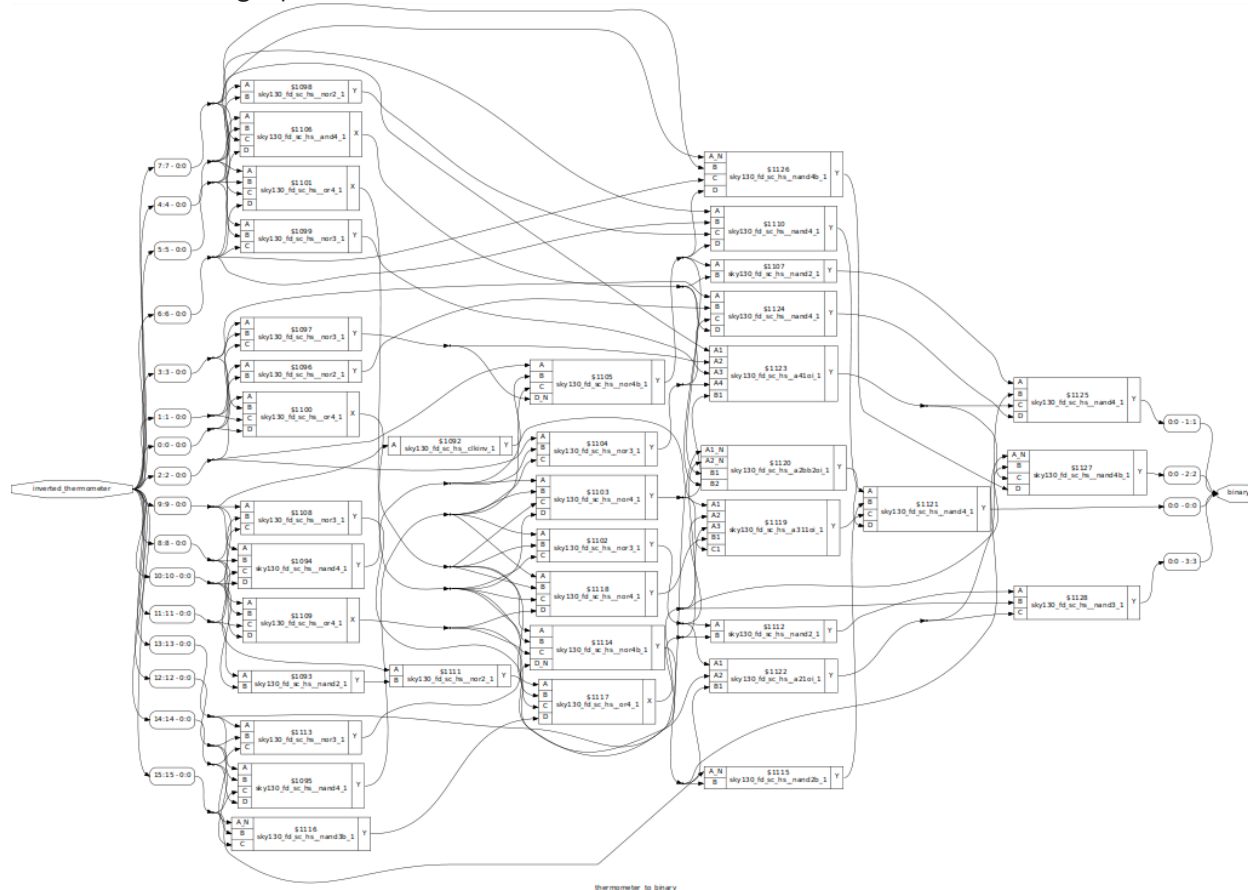

```
>> write_verilog therm.v // write the generated netlist to a new module/verilog file for verification
```

Or


```
>> write_verilog -noattr therm.v // // to write verilog netlist without attributes(clean)
```

Optimize:

```
>> flatten
```

```
>> opt_clean -purge // running optimization
```

```
>> show
```

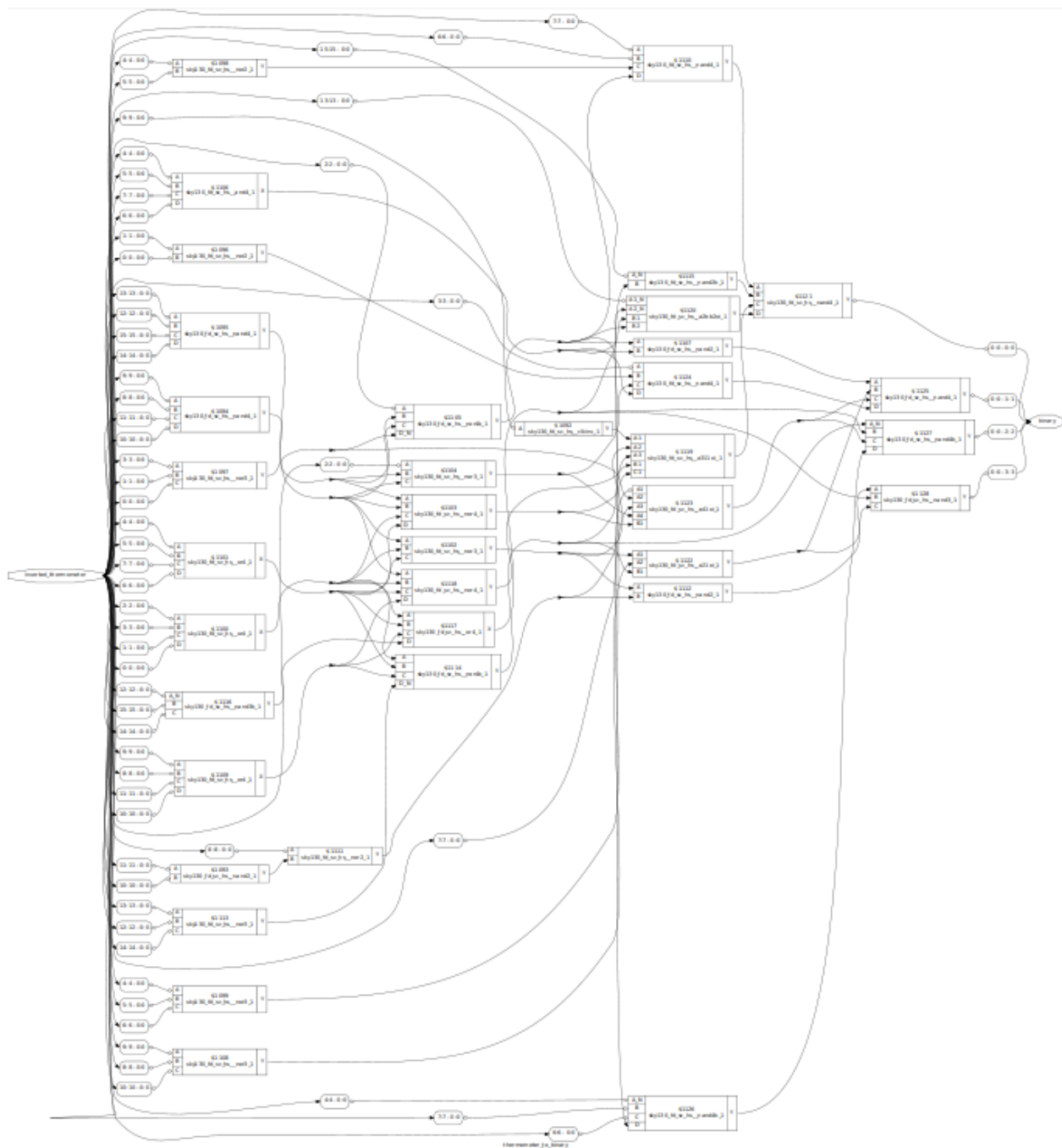

```
>> abc -liberty
/usr/local/share/pdk/sky130A/libs.ref/sky130_fd_sc_hs/lib/sky130_fd_sc_hs__tt_025C_1v89.lib
```

- simulate the complete (ultra small) ADC

References:

<https://github.com/bluecmd/learn-sky130/blob/main/schematic/xschem/getting-started.md>

---

**Run iverilo/icarus**

iverilog file.v

vvp a.out

---